



集成电路原理与设计

10. 运算放大器

宋爽

shuangsonghz@zju.edu.cn

Assignment 2

2-1 The circuit shown in Fig.2.1 illustrates a single-channel MOS resistor with a W/L of $2\mu\text{m}/2\mu\text{m}$. Using Table.2.1 model parameters calculate the small-signal on-resistance of the MOS transistor at various values for V_S and fill in the table below. (Note that the transistor was in linear region, $V_B=0$, $I_{DS}=0$)

 


Fig.2.1

$V_S(\text{V})$	$R(\Omega)$
0.0	
1.0	
2.0	
3.0	
4.0	
5.0	

Answer

The equation for threshold voltage is represented with absolute values so that it can be applied to n-channel or p-channel transistors without confusion.

$$|V_T| = |V_{T0}| + \gamma[\sqrt{2|\Phi_F| + |V_{SB}|} - \sqrt{2|\Phi_F|}]$$

$$r_{on} = \frac{1}{\partial I_D / \partial V_{DS}} = \frac{L}{KW(|V_{GS}| - |V_T| - |V_{DS}|)}$$

For n-channel device

$$V_{T0} = 0.7, \gamma = 0.45, 2|\Phi_F| = 0.9, K = 134$$

(1) When $V_S = 0, V_{GS} = 5$ and $V_{SB} = 0$

$$|V_T| = |V_{T0}| + \gamma[\sqrt{2|\Phi_F| + |V_{SB}|} - \sqrt{2|\Phi_F|}] = 0.7$$

$$r_{on} = \frac{1}{\partial I_D / \partial V_{DS}} = \frac{L}{KW(|V_{GS}| - |V_T| - |V_{DS}|)} = 1.736K\Omega$$

(2) When $V_S = 1, V_{GS} = 4$ and $V_{SB} = 1$

$$|V_T| = |V_{T0}| + \gamma[\sqrt{2|\Phi_F| + |V_{SB}|} - \sqrt{2|\Phi_F|}] = 0.893$$

$$r_{on} = \frac{1}{\partial I_D / \partial V_{DS}} = \frac{L}{KW(|V_{GS}| - |V_T| - |V_{DS}|)} = 2.402K\Omega$$

(3) When $V_S = 2, V_{GS} = 3$ and $V_{SB} = 2$

$$|V_T| = |V_{T0}| + \gamma[\sqrt{2|\Phi_F| + |V_{SB}|} - \sqrt{2|\Phi_F|}] = 1.039$$

$$r_{on} = \frac{1}{\partial I_D / \partial V_{DS}} = \frac{L}{KW(|V_{GS}| - |V_T| - |V_{DS}|)} = 3.806K\Omega$$

(4) When $V_S = 3, V_{GS} = 2$ and $V_{SB} = 3$

$$|V_T| = |V_{T0}| + \gamma[\sqrt{2|\Phi_F| + |V_{SB}|} - \sqrt{2|\Phi_F|}] = 1.162$$

$$r_{on} = \frac{1}{\partial I_D / \partial V_{DS}} = \frac{L}{KW(|V_{GS}| - |V_T| - |V_{DS}|)} = 8.905K\Omega$$

(5) When $V_S = 4, V_{GS} = 1$ and $V_{SB} = 4$

$$|V_T| = |V_{T0}| + \gamma[\sqrt{2|\Phi_F| + |V_{SB}|} - \sqrt{2|\Phi_F|}] = 1.269$$

$V_{GS} < V_T$. The device is cutoff, so $r_{on} = \text{infinity}$

(6) When $V_S = 5, V_{GS} = 0$ and $V_{SB} = 5$

The device is cutoff, so $r_{on} = \text{infinity}$

$V_S(\text{V})$	$R(\Omega)$
0.0	1.736K
1.0	2.402K
2.0	3.806K
3.0	8.905K
4.0	infinity
5.0	infinity

Assignment 2

3-2. An NMOS with $W=50\mu\text{m}$ and $L=0.5\mu\text{m}$ operates in the **saturated region** and its layout is folded shown as Fig3.2. Calculate the all capacitances by using the parameters in Table3.2 and $C_{ox}=3.8\times 10^{-3}\text{F/m}$, $V_R=0.6\text{V}$. Assume that the minimum size (lateral) of S/D region is $1.5\mu\text{m}$.

 


Fig.3.2

Answer:

$$C_{j0} = 0.56 \times \frac{10^{-3}\text{F}}{\text{m}^2}, C_{j\text{sw}0} = 0.35 \times \frac{10^{-11}\text{F}}{\text{m}}, m_j = 0.45, m_{j\text{sw}} = 0.2$$

$$C_{ov} = 0.4 \times \frac{10^{-9}\text{F}}{\text{m}}, W = 50\mu\text{m}, L = 0.5\mu\text{m}, L_D = 0.08\mu\text{m}, E = 1.5\mu\text{m}$$

$$V_R = 0.6\text{V}, 2\Phi_F = 0.9\text{V}, C_{ox} = 3.8 \times 10^{-3}\text{F/m}^2, P_{SUB} = 9 \times 10^8\text{m}^{-3}$$

$$\epsilon_{sl} = 11.7 \times 8.85 \times 10^{-12}\text{F/m}, q = 1.6 \times 10^{-19}\text{C}$$

$$C_j = \frac{C_{j0}}{(1 + V_R/2\Phi_F)^{m_j}} = 0.445 \text{ fF}/\mu\text{m}^2, C_{j\text{sw}} = \frac{C_{j\text{sw}0}}{(1 + V_R/2\Phi_F)^{m_{j\text{sw}}}} = 3.16 \times \frac{10^{-3}\text{fF}}{\mu\text{m}}$$

$$L_{eff} = L - 2L_D = 0.34 \mu\text{m}, C_d = WL_{eff}\sqrt{q\epsilon_{sl}P_{SUB}/4\Phi_F} = 1.55 \times 10^{-6}\text{fF}$$

$$C_{DB} = \frac{W}{2}EC_j + 2\left(\frac{W}{2} + E\right)C_{j\text{sw}} = 16.85\text{fF}$$

$$C_{SB} = 2\left(\frac{W}{2}EC_j + 2\left(\frac{W}{2} + E\right)C_{j\text{sw}}\right) = 33.71\text{fF}$$

$$C_{GD} = 2\left(\frac{W}{2}C_{ov}\right) = 20.0\text{fF}$$

$$C_{GS} = \frac{2}{3}WL_{eff}C_{ox} + WC_{ov} = 63\text{fF}$$

$$C_{GB} = \frac{WL_{eff}C_{ox}C_d}{(WL_{eff}C_{ox} + C_d)} = 1.55 \times 10^{-6}\text{fF}$$

Table.3.1

Typical Parameter Value				
Parameter Symbol	Parameter Description	n-Channel	p-Channel	Units
V_{T0}	Threshold voltage ($V_{BS}=0$)	0.7	-0.8	V
K	Transconductance parameter (in saturation)	134	50	$\mu\text{A}/\text{V}^2$
γ	Bulk threshold parameter	0.45	0.4	$\text{V}^{1/2}$
λ	Channel length modulation parameter	0.1	0.2	V^{-1}
$2 \phi_F $	Surface potential at strong inversion	0.9	0.8	V



Table.3.2

NMOS Model			
LEVEL=1	VTO=0.7	GAMMA=0.45	PHI=0.9
PSUB=9e+14	LD=0.08e-6	UO=350	LAMBDA=0.1
TOX=9e-9	PB=0.9	CJ=0.56e-3	CJSW=0.35e-11
MJ=0.45	MJSW=0.2	CGDO=0.4e-9	JS=1.0e-8
PMOS Model			
LEVEL=1	VTO=-0.8	GAMMA=0.4	PHI=0.8
PSUB=5e+14	LD=0.09e-6	UO=100	LAMBDA=0.2
TOX=9e-9	PB=0.9	CJ=0.94e-3	CJSW=0.32e-11
MJ=0.5	MJSW=0.3	CGDO=0.3e-9	JS=0.5e-8

上表给出的是 $0.5\mu\text{m}$ 工艺 level-1 MOS-SPICE 模型参数的典型值，其中的参数定义如下：

VTO:	→	VS _B =0 时的阈值电压	→	(单位: V)
GAMMA:	→	体效应系数	→	(单位: V ^{1/2})
PHI:	→	2Φ _F	→	(单位: V)
TOX:	→	栅氧厚度	→	(单位: m)
NSUB:	→	衬底掺杂浓度	→	(单位: cm ⁻³)
LD:	→	源/漏侧扩散长度	→	(单位: m)
UO:	→	沟道迁移率	→	(单位: cm ² /(v·s))
LAMBDA:	→	沟道长度调制系数	→	(单位: V ⁻¹)
CJ:	→	单位面积的源/漏结电容	→	(单位: F/m ²)
CJSW:	→	单位长度的源/漏侧壁结电容	→	(单位: F/m)
PB:	→	源/漏结内建电势	→	(单位: V)
MJ:	→	CJ 公式中的幂指数	→	(无单位)
MJSW:	→	CJSW 等式中的幂指数	→	(无单位)
CGDO:	→	单位宽度的栅/漏交叠电容	→	(单位: F/m)
CGSO:	→	单位宽度的栅/源交叠电容	→	(单位: F/m)
JS:	→	源/漏结单位面积的漏电流	→	(单位: A/m ²)

MOS Device Capacitance: Depletion Cap

  

$$C_{BX} = \frac{(CJ)(AS)}{\left[1 - \left(\frac{V_{BX}}{PB}\right)\right]^{MJ}} + \frac{(CJSW)(PS)}{\left[1 - \left(\frac{V_{BX}}{PB}\right)\right]^{MJSW}}$$

*Bottom-plate
Capacitance
(per area)*

*Side-wall
capacitance
(per perimeter)*

X: "S" or "D"

AS=area of the source

PS=perimeter of the source

CJSW=zero bias, bulk-source sidewall capacitance

MJSW=bulk-source sidewall grading coefficient

Assignment 2

2-3→ There is an N-type current source, I_D is 0.5mA, and the drain-source voltage V_{DS} must more than 0.4V when it works as a current source. If the minimum output resistance is 20 K Ω , determine the length and width of the device by using the parameters in Table.2.2.

↵
Answer: ↵

$$\begin{cases} r_o = \frac{1}{\lambda I_D} = 20K\Omega \\ I_D = 0.5mA \end{cases} \Rightarrow \lambda = 0.1 \text{ ↵}$$

From the table 3.2, L can be determined as $L = 0.5\mu m$. (↵

$$L_{eff} = L - 2L_D = 0.5\mu m - 2 \times 0.08\mu m = 0.34\mu m \text{ ↵}$$

Calculating W ↵

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L_{eff}} (V_{GS} - V_{TH})^2, \quad V_{GS} - V_{TH} = V_{DSAT} = 0.4V \text{ ↵}$$

$$\frac{W}{L_{eff}} = \frac{I_D}{\frac{1}{2} \mu_n C_{ox} (V_{GS} - V_{TH})^2} = \frac{0.5 \times 10^{-3}}{\frac{1}{2} \times 134 \times 10^{-6} \times 0.4^2} = 46.64 \text{ ↵}$$

$$\therefore W = 46.64 L_{eff} = 15.86\mu m \text{ ↵}$$

Assignment 2

2-4→ A “ring” MOS structure is shown in Fig.2.3. Explain how the device operations and estimate its equivalent aspect ratio. Calculate the drain junction capacitance of the structure. (use C_j and C_{jsw}) ↵

 


Fig.2.3 ↵

Answer: ↵

→ → Width/length ratio is $4W/L$ ↵

→ → $C_{DB} = W^2 C_j + 4WC_{jsw}$ ↵

Assignment 2

2-5 Find the small-signal model (g_m , g_{mb} , g_{ds}) for an n-channel transistor with the drain at 4 V, gate at 4 V, source at 2 V, and the bulk at 0 V. Assume the model parameters from Table 2.1, and $W/L = 10 \mu\text{m}/1 \mu\text{m}$.

Answer:

$$V_T = V_{T0} + \gamma \left[\sqrt{2|\Phi_F| + v_{SB}} - \sqrt{2|\Phi_F|} \right]$$

$$V_T = 0.7 + 0.45 \left[\sqrt{0.9 + 2.0} - \sqrt{0.9} \right] = 1.04 \text{ V}$$

$$I_D = \frac{KW}{L} (v_{GS} - v_T)^2 (1 + \lambda v_{DS})$$

$$I_D = 134 \times 10^{-6} \times 10 \times (2 - 1.04)^2 (1 + 0.1 \times 2) = 1482 \times 10^{-6} \text{ A}$$

$$g_m = \sqrt{4 \frac{KW}{L} I_D}$$

$$g_m = \sqrt{4 \times 134 \times 10^{-6} \times 10 \times 1482 \times 10^{-6}} = 2.818 \times 10^{-3} \text{ S}$$

$$g_{mb} = g_m \frac{\gamma}{2(2|\Phi_F| + V_{SB})^{\frac{1}{2}}}$$

$$g_{mb} = 2.818 \times 10^{-3} \frac{0.45}{2(0.9 + 2.0)^{\frac{1}{2}}} = 372.3 \times 10^{-6} \text{ S}$$

$$g_{ds} = \frac{\lambda I_D}{1 + \lambda V_{DS}}$$

$$g_{ds} = 1482 \times 10^{-6} \times 0.1 \div 1.2 = 123.5 \times 10^{-6} \text{ S}$$



Course Arrangements

课数	内容	课数	内容
1	导论	9	差分放大器
2	工艺流程	10	运算放大器
3	器件模型一	11	逻辑门
4	器件模型二	12	组合逻辑
5	模拟基本单元	13	时序逻辑
6	电流镜与基准	14	加法器/乘法器
7	单级放大器	15	集成电路专题讲座一
8	课堂测验	16	集成电路专题讲座二




Outline

- ☐ **General Consideration**
- ☐ **One-Stage Op Amps**
- ☐ **Two-Stage Op Amps**
- ☐ **Compensation of 2-Stage Op Amps**
- ☐ **Other Issues of Op Amps**


Why it is called Op. Amp

 For different operations based on feedbacks




Noninverting amplifier

$$G_V^* = (R_1 + R_2) / R_1$$

 

Inverting amplifier

$$G_V^* = R_2 / R_1$$


 


Voltage follower

$$G_V^* = 1$$


Why it is so important

In signal chain applications: (IA+ADC)

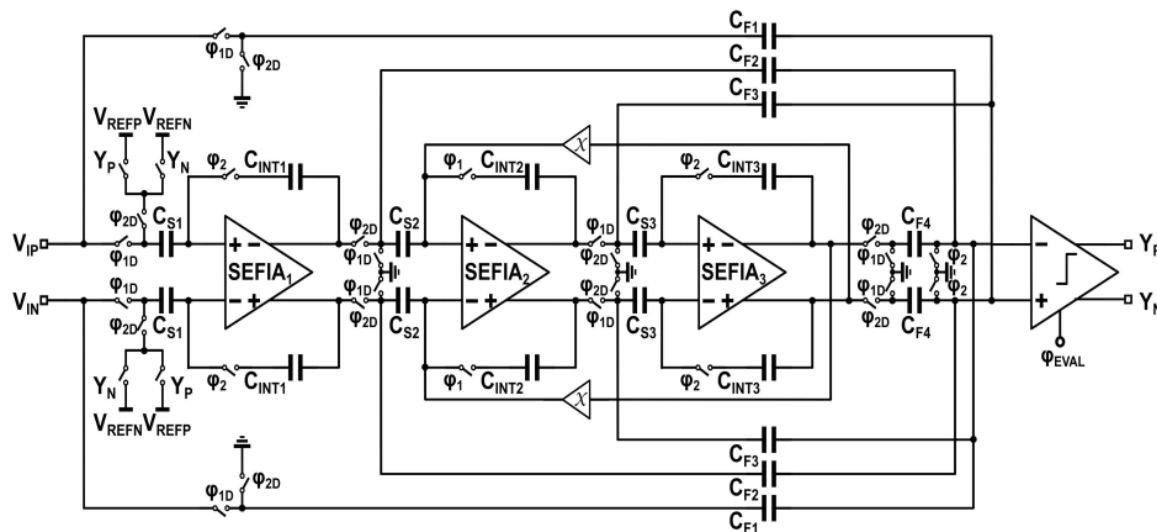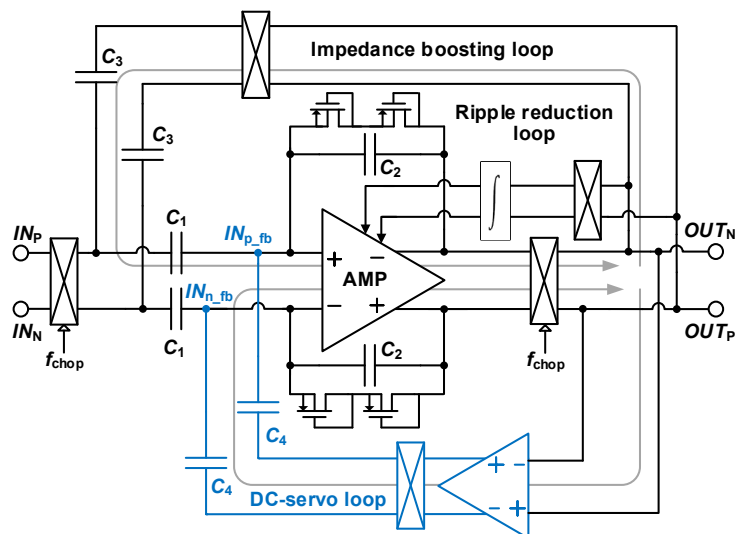

Why it is so important

In power management applications:

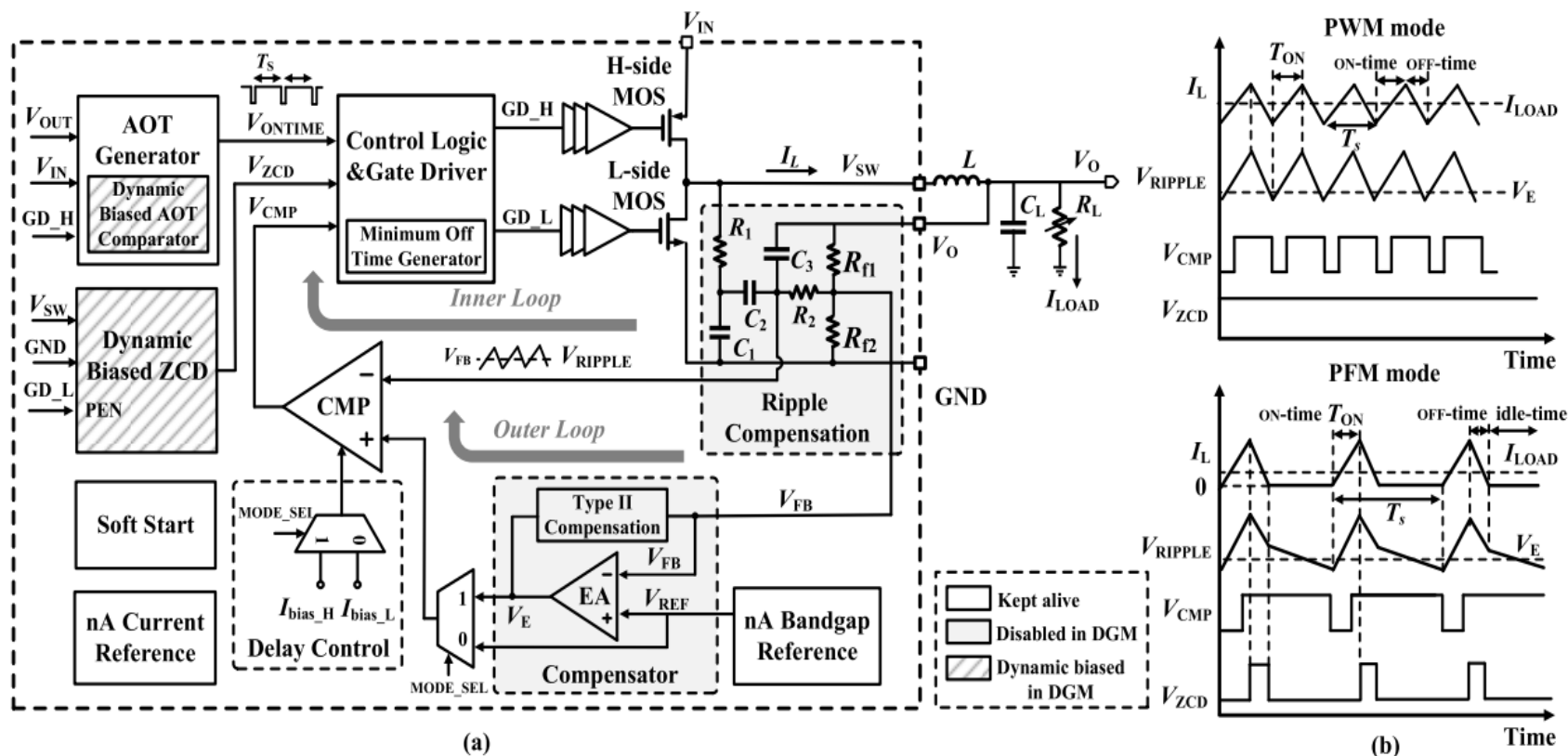


Basic Concept of Op Amp

A high-gain differential amplifier

□ Ideal op amp

 - Voltage controlled voltage source
- **Infinite** gain
- Infinite **input** impedance
- Zero **output** impedance
- Infinite CMRR and PSRR



□ Application

- DC generation
- Amplification
- Integration/Differentiation
- Filtering (HP/LP/BP)

If the infinite differential gain, then


$$v_1 - v_2 = v_i = 0$$

$$i_1 = 0 \text{ and } i_2 = 0$$

The differential input voltage is zero and no current flow into or out of the differential input

Feedback

Nonideal model of Op amp

 

where

R_{id} = differential input resistance

C_{id} = differential input capacitance

R_{icm} = common mode input resistance

V_{OS} = input-offset voltage

I_{B1} and I_{B2} = differential input-bias currents

I_{OS} = input-offset current ($I_{OS} = I_{B1} - I_{B2}$)

$CMRR$ = common-mode rejection ratio

e_n^2 = voltage-noise spectral density (mean-square volts/Hertz)

i_n^2 = current-noise spectral density (mean-square amps/Hertz)



Performance Parameters

□ Gain

- Open-loop gain: DC条件下, 在输入加一小信号, 得到输出电压

$$A_d = 10 \sim 10^5 \text{ (20dB} \sim 100\text{dB)}$$

$$\text{High gain: } A_d \sim 80\text{dB} - 100\text{dB}$$


- Common-mode Gain: 在输入加共模小信号, 得到输出电压

$$A_{CM} \sim 20\text{dB} - 40\text{dB}$$

- CMRR(Common-mode Rejection Ratio)

$$\text{CMRR} \sim 40\text{dB} - 80\text{dB}$$

Example Non-inverting Voltage Amplifier.

 

- ❑ Input and output swing: rail-to-rail
- ❑ Amplifier buffer
- ❑ **High open-gain could suppress nonlinearity**

Close-loop Gain: $\left(V_{in} - \frac{R_2}{R_1 + R_2} V_{out} \right) A_1 = V_{out}$

$$\begin{aligned} \frac{V_{out}}{V_{in}} &= \frac{A_1}{1 + \frac{R_2}{R_1 + R_2} A_1} = \frac{R_1 + R_2}{R_2} \frac{A_1}{1 + \frac{R_1 + R_2}{R_2} A_1} \approx \left(1 + \frac{R_1}{R_2} \right) \left(1 - \frac{R_1 + R_2}{R_2} \frac{1}{A_1} \right) \\ &= \frac{1}{\beta} \left(1 - \frac{1}{\beta A_1} \right) \xrightarrow{\beta A_1 \rightarrow \infty} \frac{1}{\beta} \end{aligned}$$

Feedback coefficient: $\beta = \frac{R_2}{R_1 + R_2}$

Loop gain: βA_1

Relative gain error: $\frac{1}{\beta A_1}$

The circuit has a nominal gain of 10. i.e., $1 + R_1/R_2 = 10$
 If a gain error $< 1\%$ $\Rightarrow A_1 > 1000$

Higher open gain \rightarrow smaller gain error

Small-signal behavior of frequency response



□ Differential and common-mode frequency response

$$V_{out}(s) = A_d(s) [V_1(s) - V_2(s)] \pm A_c(s) \left(\frac{V_1(s) + V_2(s)}{2} \right)$$

□ Differential-frequency response:

$$A_d(s) = \frac{A_{d0}}{\left(\frac{s}{p_1} - 1 \right) \left(\frac{s}{p_2} - 1 \right) \left(\frac{s}{p_3} - 1 \right) \dots} = \frac{A_{d0} p_1 p_2 p_3 \dots}{(s - p_1)(s - p_2)(s - p_3) \dots}$$

where p_1, p_2, p_3, \dots are the poles of the differential-frequency response (ignoring zeros)

 


Fig. 110-06

□ Bandwidth: BW

□ Unity-Gain frequency: GB $f_u \rightarrow w_u$

□ -3dB frequency: $f_{-3dB} \rightarrow w_1$

Large-signal behavior of frequency response




在瞬态输入**大信号**工作时，表征运放的速度：

- 转换速率 SR (Slew Rate)

- SR = output voltage rate limit of the op amp

 - 建立时间 T_s (Settling time, usually $<1\%$)







Example

Assume the op amp is a single-pole voltage amplifier and V_{in} is a small step input. Calculate the time for V_{out} to reach within 1% and the unity-gain bandwidth if $1+R_1/R_2=10$ and the settling time $<5ns$.

Solution: Speed vs. Bandwidth

For a single-pole amp:

$$A(s) = \frac{A_0}{(1 + s/\omega_0)}$$

  

$$\frac{V_{out}}{V_{in}}(s) = \frac{A(s)}{1 + \frac{R_2}{R_1 + R_2} A(s)} = \frac{A_0 / (1 + A_0 \beta)}{1 + \frac{s}{(1 + A_0 \beta) \omega_0}}$$

Bandwidth expanding

$$\tau = \frac{1}{(1 + A_0 \beta) \omega_0} \approx \left(1 + \frac{R_1}{R_2}\right) \frac{1}{A_0 \omega_0}$$

$$V_{in} = au(t) \quad \longrightarrow \quad V_{out} = a \left(\frac{A_0}{1 + \beta A_0} \right) \left(1 - \exp \frac{-t}{\tau} \right) u(t)$$

For 1% settling: $V_{out} = 0.99V_F$ $1 - \exp \frac{-t_{1\%}}{\tau} = 0.99 \quad \longrightarrow \quad t_{1\%} = \tau \ln 100 = 4.6\tau < 5ns$
 $\tau \approx 1.09ns$

$$A_0 \omega_0 \approx (1 + R_1/R_2) / \tau = 9.21 \text{ Grad/s} \quad (1.47GHz)$$

For 0.1% settling: $t_{0.1\%} = \tau \ln 1000 = 6.9\tau$



Performance Parameters

- **Output Swing**: output voltage range without distortion
- **ICMR**: (Input Common Mode Range)
 - ICMR= the voltage range over which the input common-mode signal can vary without influence the differential performance
- **Linearity**: input-pair exhibit a nonlinear relation between its differential drain current and its input voltage
- **PSRR**: (Power Supply Rejection Ration)
$$PSRR = \frac{\Delta V_{DD}}{\Delta V_{OUT}} A_V(s) = \frac{V_O/V_{in} (V_{dd} = 0)}{V_O/V_{dd} (V_{in} = 0)}$$
- **Offset**: the minimum signal level that can be processed with reasonable quality
- **Noise**


Specifications for a typical unbuffered CMOS Op Amp



Boundary Conditions	Requirement
Process Specification	See Tables 3.1-1 and 3.1-2
Supply Voltage	$\pm 2.5 \text{ V} \pm 10\%$
Supply Current	$100 \mu\text{A}$
Temperature Range	$0 \text{ to } 70^\circ\text{C}$
Specifications	Value
Gain	$\geq 70 \text{ dB}$
Gainbandwidth	$\geq 5 \text{ MHz}$
Settling Time	$\leq 1 \mu\text{sec}$
Slew Rate	$\geq 5 \text{ V}/\mu\text{sec}$
Input <i>CMR</i>	$\geq \pm 1.5 \text{ V}$
<i>CMRR</i>	$\geq 60 \text{ dB}$
<i>PSRR</i>	$\geq 60 \text{ dB}$
Output Swing	$\geq \pm 1.5 \text{ V}$
Output Resistance	N/A, capacitive load only
Offset	$\leq \pm 10 \text{ mV}$
Noise	$\leq 100 \text{ nV}/\sqrt{\text{Hz}}$ at 1KHz
Layout Area	$\leq 10,000 \text{ min. channel length}^2$

AMP and OTA

 Inverting Voltage Amplifier $V_{inp} = 0$



□ Input common mode: a fixed voltage

□ Input range could be small, but the output range could be rail-to-rail

$$A \rightarrow \infty \quad A_V = \frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$$

Operational Transconductance Amplifiers (OTAs)



- Driving capacitive load G_m stage
- High gain : **high output resistance**
- Generally be used in switched-capacitor (SC) circuits



Outline

- ☐ General Consideration
- ☐ **One-Stage Op Amps (First Stage of Opamps)**
- ☐ Two-Stage Op Amps
- ☐ Compensation of 2-Stage Op Amps
- ☐ Other Issues of Op Amps

Basic Topologies

  

- Low-frequency gain: $A_O = g_{mN} r_{out} = g_{mN} (r_{ON} // r_{OP}) < g_{mN} r_O$
- Bandwidth: $\omega_1 = \frac{1}{C_L R_{out}} = \frac{1}{(r_{O2} // r_{O4}) C_L} \quad \omega_u = \frac{g_{mN}}{C_L}$
- Output Swing (single-side): $V_{DD} - 3V_{OV}$
- Mirror pole in single ended

Example

Calculate the input common-mode voltage range and the closed-loop output impedance of **the unity-gain buffer**.



Input common-mode voltage range

All transistors operate saturation region

$$V_{in,min} = V_{ISS} + V_{GS1} = V_{ISSds,sat} + V_{th1} + V_{ds,sat1} = 0.1 + 0.3 + 0.1 = 0.5V$$

$$V_{in,max} = V_{DD} - (|V_{GS3}| + V_{th1}) = 1 - (0.1 + 0.3) = 0.9V$$

$$V_{in,max} - V_{in,min} = V_{DD} - |V_{th3}| - 3V_{ds,sat} = 0.4V$$

  

Output resistance

■ The open-loop output impedance: $r_{O2} // r_{O4}$

■ Loop gain: $g_{m1} (r_{O2} // r_{O4})$

■ The closed-loop output impedance : $\frac{r_{O2} // r_{O4}}{1 + g_{m1} (r_{O2} // r_{O4})} \approx \frac{1}{g_{m1}}$

Voltage feedback at output

□ The closed-loop pole is independent of open-loop output impedance.

Telescopic Cascode Op Amps

High gain!!! $\times 20 \sim 40$

Small output swing!!!

□ Low-frequency gain:

$$A_O = g_{m2} R_{out} = g_{m2} (g_{m4} r_{O2} r_{O4} // g_{m6} r_{O6} r_{O8})$$

$$\approx g_{mN} (g_{mN} r_{ON}^2 // g_{mP} r_{OP}^2)$$

□ Output Swing (single-side):

$$V_{DD} - 5V_{OV}$$



□ Speed:

■ Dominant pole

■ Additional poles X in high frequency

■ Mirror pole in single-ended

 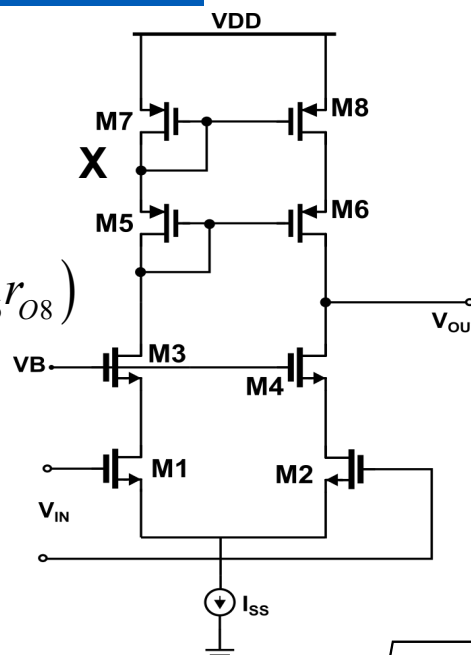□ Be difficult to short telescopic OPAMP output to input (why)





Telescopic Cascode Op Amps

Input common-mode voltage range

All transistors operate saturation region

$$V_{in,min} = V_{ds,sat,ISS} + V_{GS2} = V_{ds,sat,ISS} + V_{th2} + V_{ds,sat2}$$

$$V_{in,max} = V_{b1} - |V_{GS3}| + V_{th2}$$

➔ $V_{in,max} - V_{in,min} = V_{b1} - V_{th4} - 3V_{ds,sat}$

$$V_{b1} > V_{th4} + 3V_{ds,sat}$$

Output common-mode voltage range


All transistors operate saturation region

$$V_{out,min} = V_{b1} - V_{th4}$$

$$V_{out,max} = V_{b2} + |V_{th6}|$$

Output swings: $2(V_{out,max} - V_{out,min}) = 2(V_{b2} + |V_{th6}| - V_{b1} - V_{th2})$
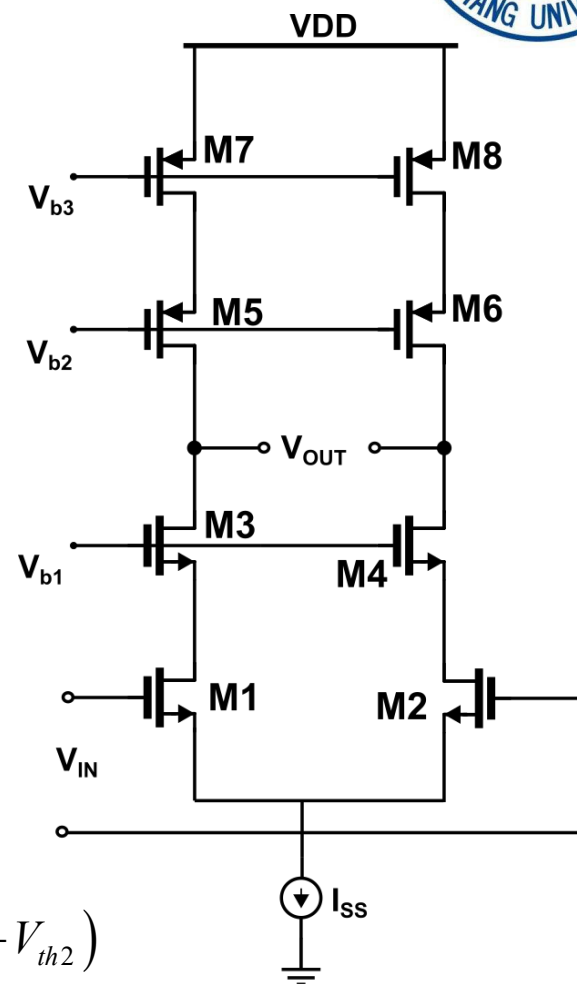
$$V_{b2} \uparrow, V_{b1} \downarrow \Rightarrow \text{output range} \uparrow$$



极限值 $\rightarrow 2(V_{DD} - V_{ds8,sat} - V_{ds6,sat} - V_{ds4,sat} - V_{ds2,sat} - V_{ISS,ds,sat}) = 2(V_{DD} - 5V_{ds,sat})$ 27

Output common-mode voltage range of unity-gain buffer

All transistors operate saturation region

M2: $V_{out,max} = V_x + V_{th2} = V_b - V_{GS4} + V_{th2}$


M4: $V_{out,min} = V_b - V_{ds4,sat}$

$$V_b - V_{th4} \leq V_{out} \leq V_b - V_{GS4} + V_{th2}$$


➔ $V_{out,max} - V_{out,min} = V_{th4} - (V_{GS4} - V_{th2}) = V_{th2} - V_{ds4,sat}$

Difficult to short telescopic op amp output to input !!!

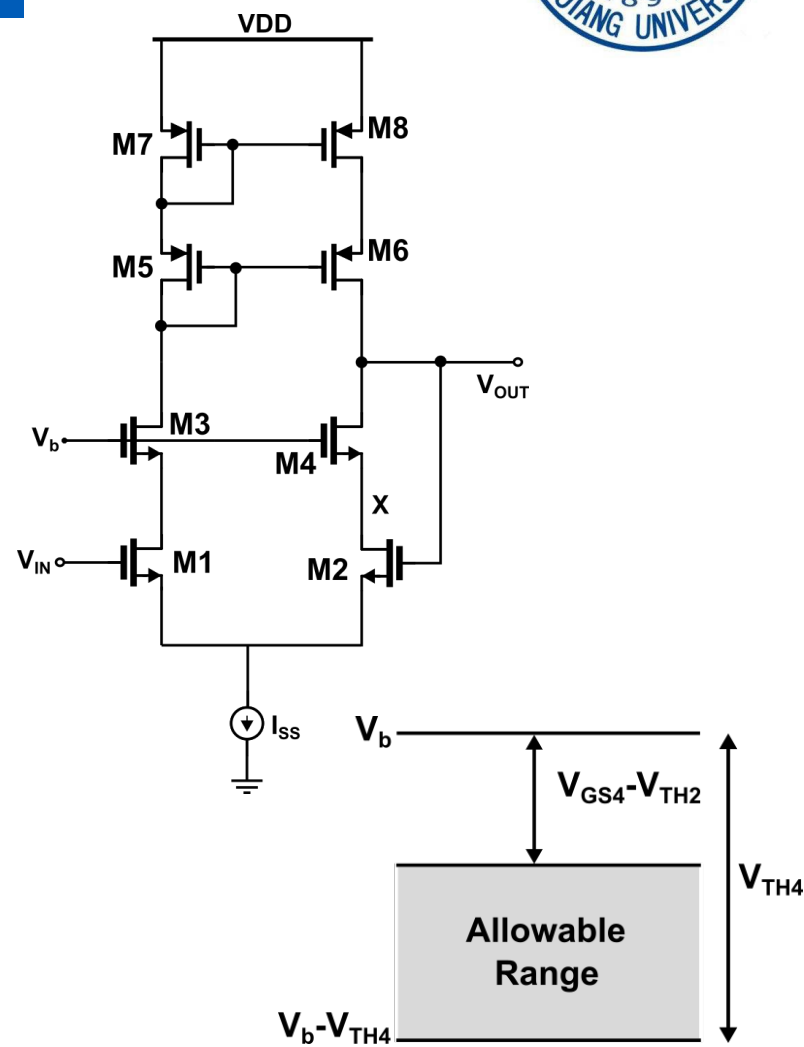High gain, small output swing ✓
Unity-gain Buffer ✗



Folded Cascode Op Amps

 


❑ Not “stack” the cascode transistor on the input device

❑ Consume higher power

$$P = V_{DD} \times (I_{SS} + I_{SS1} + I_{SS2}) > V_{DD} \times I_{SS}$$

❑ Output Voltage Swing: $V_{DD} - 4V_{OV}$

❑ Output and input could short together

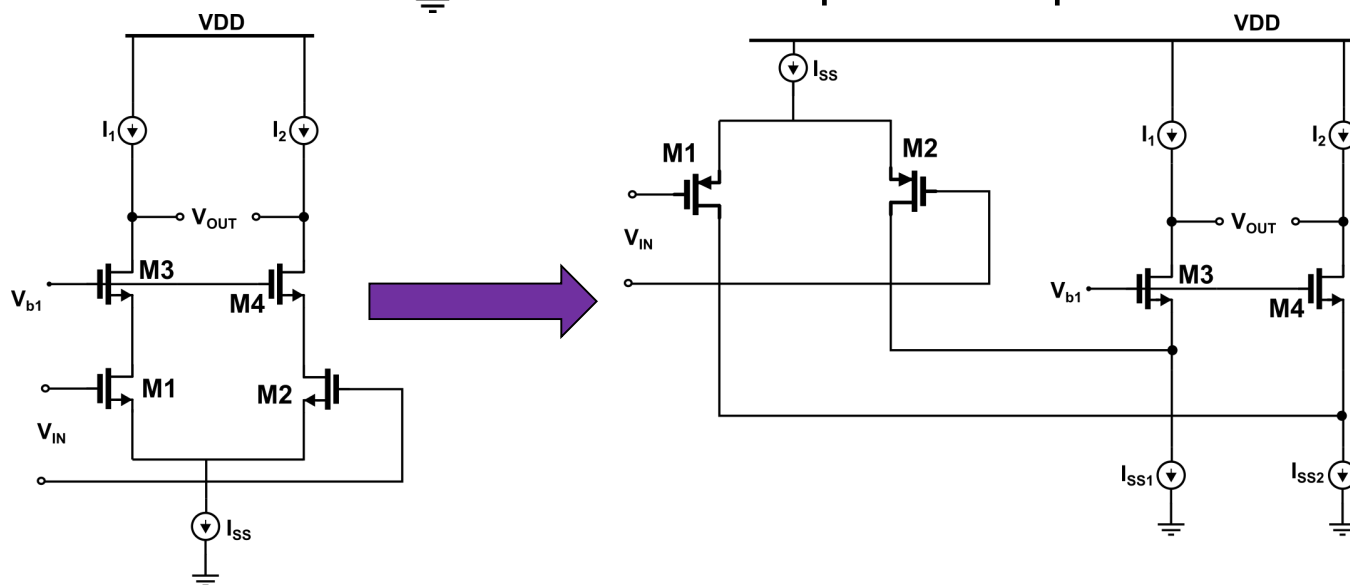

Folded Cascode Op Amps

□ Voltage Gain

$$|A_V| = G_m R_{out}$$

$$|A_V| \approx g_{m1} \left[(g_{m3} + g_{mb3}) r_{O3} (r_{O1} // r_{O5}) \right] // \left[(g_{m7} + g_{mb7}) r_{O7} r_{O9} \right]$$

□ 2~3 times **lower** than a telescopic topology

□ Input Voltage Range: **P-diff pair**


$$V_{in,min} = 0 \quad \checkmark$$

$$V_{in,max} = V_{DD} - V_{ds,sat,ISS} - V_{GS1}$$

□ Output Voltage Range

$$V_{out,min} = V_{b1} - V_{th3} \quad V_{out,min} > V_{ds3,sat} + V_{ds5,sat}$$

$$V_{out,max} = V_{b2} + |V_{th7}| \quad V_{out,max} < V_{DD} - (V_{ds7,sat} + V_{ds9,sat})$$

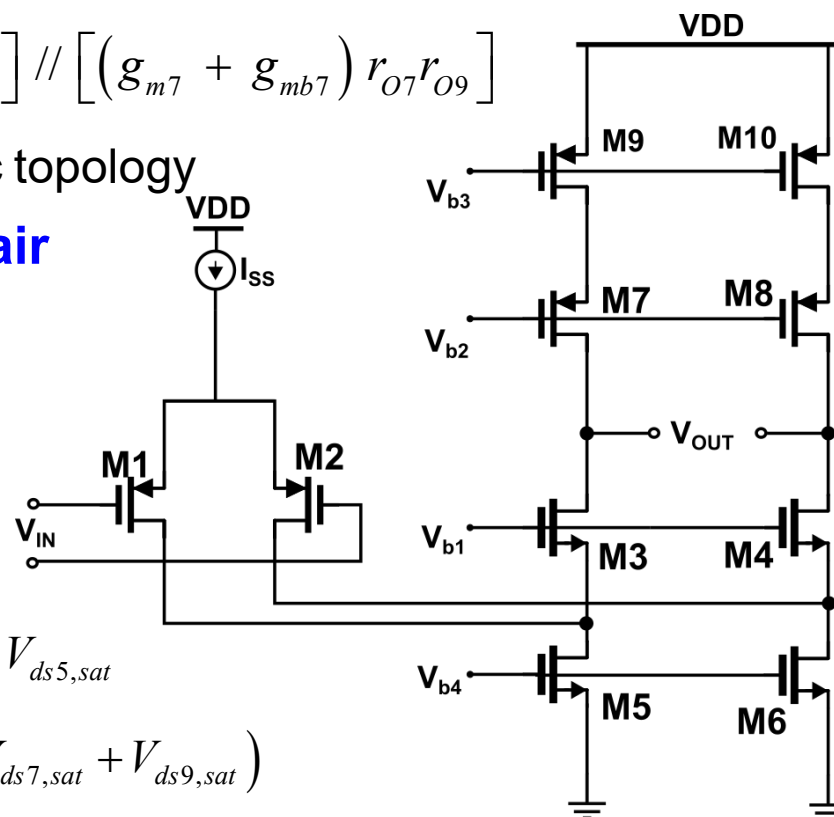



At “folding point”, a large capacitance due to a large current device M5 would be added to the total capacitance.

$$R = \frac{1}{g_{m3} + g_{mb3}}$$

$$C_{tot} = C_{GS3} + C_{SB3} + C_{DB1} + C_{GD1}$$


Input Arrangements

□ NMOS vs. PMOS Input

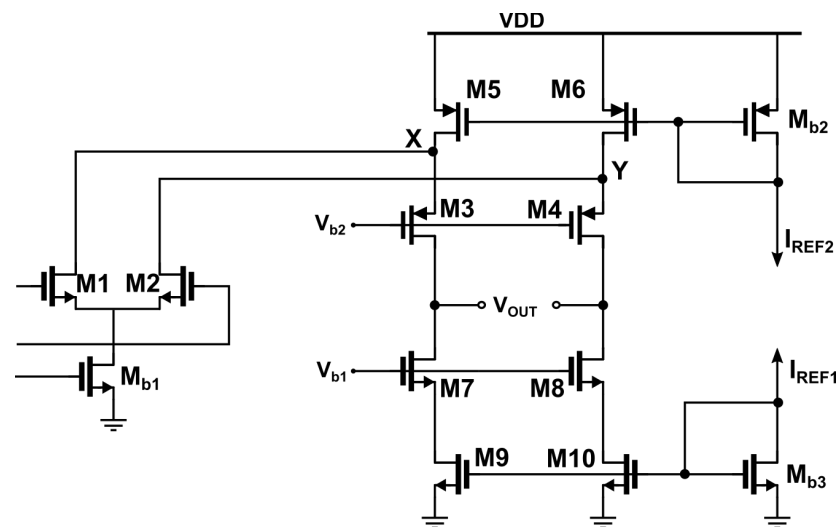 

□ Other Properties of Folded Cascode

- Slighter **Higher Output Swing** than Telescopic
- Higher power dissipation, similar voltage gain, similar pole frequency
- Input and output can be shorted: 2 overdrive from bound
- A better input CM range



Outline

- ☐ General Consideration
- ☐ One-Stage Op Amps
- ☐ **Two-Stage Op Amps**
- ☐ Compensation of 2-Stage Op Amps
- ☐ Other Issues of Op Amps

Two-Stage Op Amps

- Design limitation: low supply voltage, high gain and large output swing




Stage 1: High Gain


- Output swing could be small
- OTA

Stage 2: High Swing

 - Can we have more stages?
- Feedback stability limits !



Two-Stage Op Amps

 


$$A_V = A_{V1} \times A_{V2}$$

$$A_V = g_{m1,2} (r_{O1,2} // r_{O3,4}) g_{m5,6} (r_{O5,6} // r_{O7,8})$$

$$V_{out,min} = V_{ds7,sat}$$

$$V_{out,max} = V_{DD} - V_{ds5,sat}$$

 

$$A_V = g_{m1} (g_{m3} r_{O3} r_{O1} // g_{m5} r_{O5} r_{O7}) g_{m9} (r_{O9} // r_{O11})$$

$$V_{out,min} = V_{ds11,sat}$$


$$V_{out,max} = V_{DD} - V_{ds9,sat}$$



Outline


- ☐ General Consideration
- ☐ One-Stage Op Amps
- ☐ Two-Stage Op Amps
- ☐ Compensation of 2-Stage Op Amps
 - > Control Theory
 - > Miller compensation
- ☐ Other Issues of Op Amps

Block diagram of two-stage op-amp

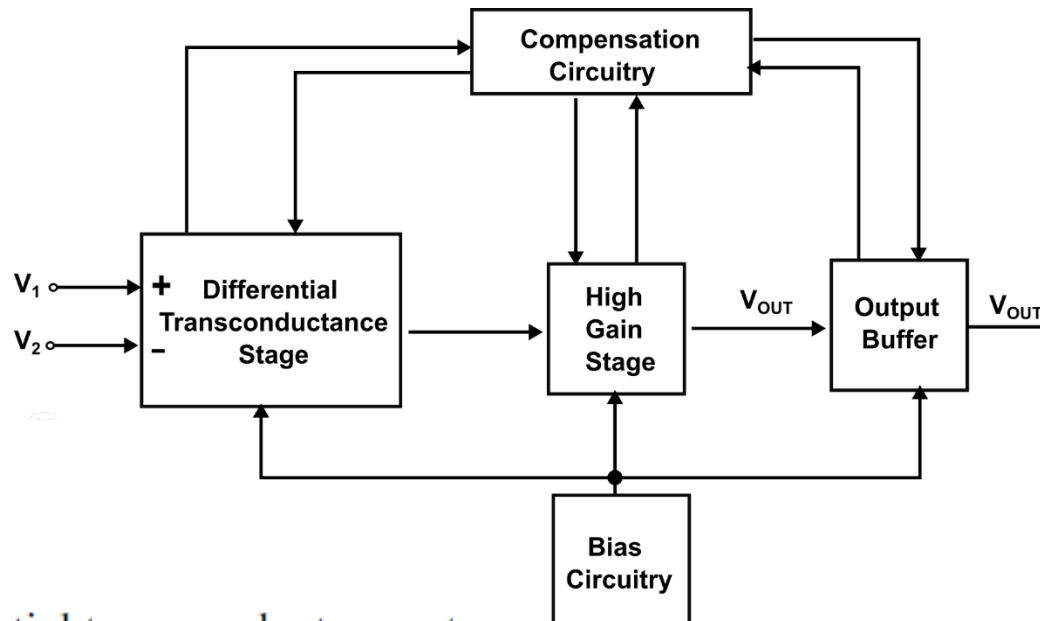

- Differential transconductance stage:
Forms the input and sometimes provides the differential-to-single ended conversion.
- High gain stage:
Provides the voltage gain required by the op amp together with the input stage.
- Output buffer:
Used if the op amp must drive a low resistance.
- Compensation:
Necessary to keep the op amp stable when resistive negative feedback is applied.


Rail to rail Folded Cascode

 

- Input Stage, Gain Stage, Output Stage
- + Bias Circuit, Frequency Compensation

General Considerations of Stability

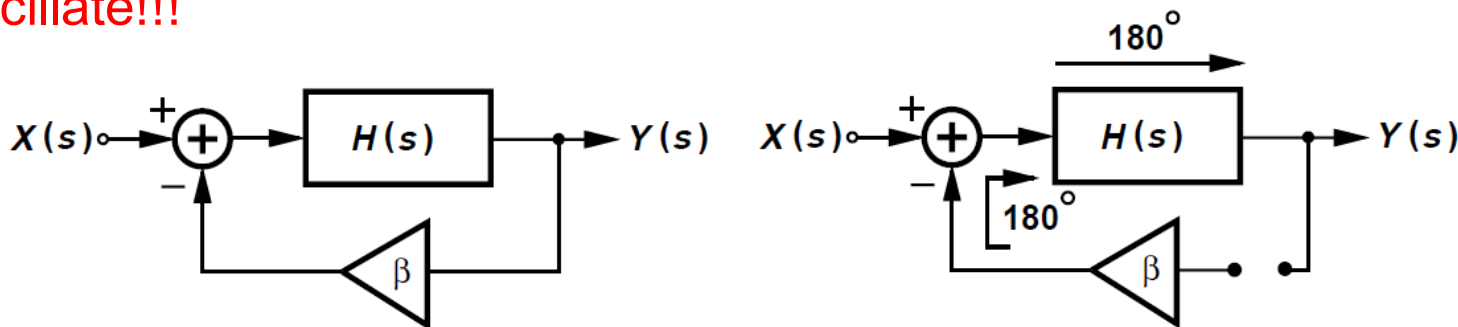- Feedback systems suffer from potential instability and they may oscillate!!!



- Closed-loop transfer function: $\frac{Y(s)}{X(s)} = \frac{H(s)}{1 + \beta H(s)}$
- When $\beta H(s) = -1$, the closed-loop “gain” goes to infinity -> oscillate
- Barkhausen’s Criteria:**


$$|\beta H(j\omega_1)| = 1$$

$$\angle \beta H(j\omega_1) = -180^\circ$$

- Negative feedback itself provides 180 phase shift

- Loop transmission determines the stability issue



Review: Bode approximation

 

- GX (Gain Crossover Point): $|gain|=1$
- PX (Phase Crossover Point): $\text{phase} = -180^\circ$

- The slope of the magnitude at zero frequency: +20dB/dec
at pole frequency: -20dB/dec.
- Zero 0.1ω : begin to change, ω : +45°, 10ω : +90°
- Pole 0.1ω : begin to change, ω : -45°, 10ω : -90°
- **The key point is that phase changes faster than magnitude.**
- The phase is much more significantly affected by high-frequency poles and zeros than the magnitude is.

  System with bode plots of loop transmission: unstable vs. stable



- Phase shift changes the negative feedback to positive

Oscillate: when phase = -180° , gain > 1




Stable: when gain = 1, phase $< -180^\circ$

- In a stable system, PX must be behind GX ($GX < PX$), and GX is equal to unity-gain bandwidth in the open-loop system

Phase Margin

$$PM = 180^\circ + \angle \beta H(\omega = \omega_2)$$

   Location of the poles on a complex plane: Root Locus




$$\beta H = \frac{1}{as^2 + bs + c}, \quad s = \sigma_p + j\omega_p$$

a term of impulse response:


$$\exp(\sigma_p + j\omega_p)$$

One-Pole System

 


Open loop: $H(s) = \frac{A_0}{1 + s/\omega_0}$

 Close loop: $\frac{Y(s)}{X(s)} = \frac{\frac{A_0}{1 + \beta A_0}}{1 + \frac{s}{\omega_0(1 + \beta A_0)}}$



□ A phase shift less than 90 °

 □ A one-pole system is unconditionally stable



□ A real-valued pole in the **left half plane**

□ Pole moves away from the origin as the loop gain β increases

Two-pole Systems


$$\omega = \omega_{p1}, \angle \beta H = -45^\circ$$

$$\omega = 10\omega_{p1}, \angle \beta H \Rightarrow -90^\circ$$


$$\omega = \omega_{p2}, \angle \beta H = -135^\circ$$

$$\omega = 10\omega_{p2}, \angle \beta H \Rightarrow -180^\circ$$

□ Stable: $PX > -180^\circ$ @GX

 

Three-Pole Systems

 

□ ω_{p3} : additional phase shift

decreases the magnitude of the loop gain at a greater rate

=> GX does not move as much as PX



=> additional poles/zeros affect the phase gristlier than they do the magnitude

Phase margin (PM)

□ How far should PX be from GX?

$$PM = 180^\circ + \angle \beta H(\omega = \omega_1 @ GX)$$

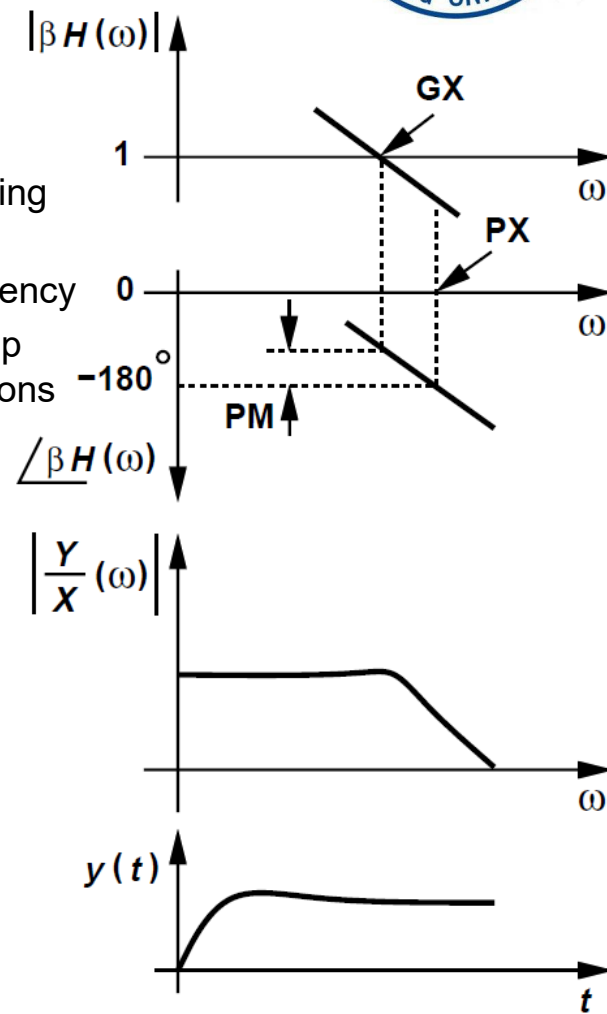 - A “well-behaved” closed-loop response concludes a greater spacing between GX and PX
- The **unity-gain bandwidth** cannot exceed the second pole frequency
- For large-signal application, time-domain simulation of closed-loop system **more relevant** and useful than small-signal as computations



Phase Margin and step response of closed loop

PM=45°





$$\frac{Y}{X}(j\omega_1) = \frac{H(j\omega_1)}{1 + 1 \times \exp(-135^\circ)} = \frac{H(j\omega_1)}{0.29 - 0.71j} = \frac{1.3}{\beta}$$

$$\left| \frac{Y}{X} \right|(\omega = \omega_1) = \frac{1}{\beta} \frac{1}{|0.29 - 0.71j|} = \frac{1.3}{\beta}$$

-- The frequency response of the feedback system suffers from a 30% peak at $\omega = \omega_1$

PM=60° $\left| \frac{Y}{X} \right| = \frac{1}{\beta}$


Trade-off

    

Phase Margin and step response of closed loop



 - ❑ For less PM, exhibits more ringing
- ❑ For greater PM, the system is more stable, **but the time response slows down**
- ❑ Generally, **PM > 45°** and the optimum value: **PM = 60°**



Trade off




Outline

- ☐ General Consideration
- ☐ One-Stage Op Amps
- ☐ Two-Stage Op Amps
- ☐ Compensation of 2-Stage Op Amps
 - > Control Theory
 - > Miller compensation
- ☐ Other Issues of Op Amps

Compensation of 2-stage Op Amps

-- Miller Compensation

 

Stage 1: High output impedance

Stage 2: A moderate gain


- **dominating pole: a large C at node E** $C_{eq} = C_E + (1 + A_{v2}) C_C$

⇒ a low frequency pole with a moderate capacitor


Miller Compensation !

$$f_{pE} = \frac{1}{2\pi R_{out1} [C_E + (1 + A_{v2}) C_C]} \approx \frac{1}{2\pi R_{out1} A_{v2} C_C}$$

 ⇒ move the output pole away from the origin




Miller Theorem

 

$$Z_1 = \frac{Z}{1 - \frac{V_Y}{V_X}} = \frac{Z}{1 - A_v}$$


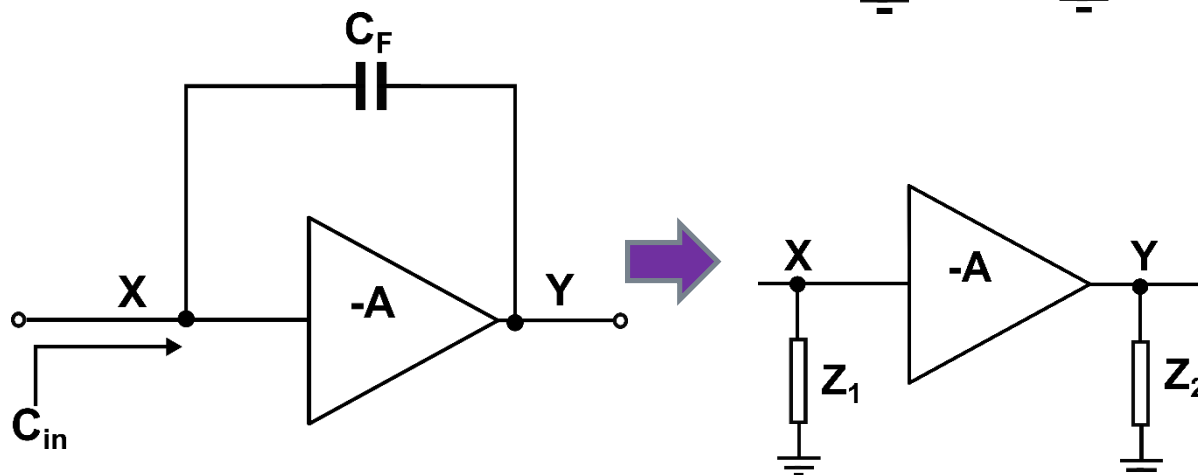
$$Z_2 = \frac{Z}{1 - \frac{V_Y}{V_X}} = \frac{Z}{1 - (A_v)^{-1}}$$



$$C_{in} = C_F (1 + A)$$

$$C_{out} = C_F (1 + A^{-1})$$

2-stage Op Amps with C_c

  

$$g_{mI} = g_{m1} = g_{m2}, R_I = r_{ds2} \parallel r_{ds4}, C_I = C_1$$

$$g_{mII} = g_{m6}, R_{II} = r_{ds6} \parallel r_{ds7}, C_{II} = C_2 = C_L$$

C_c = accomplishes the Miller compensation

C_M = capacitance associated with the first-stage mirror (mirror pole)

C_I = output capacitance to ground of the first-stage

C_{II} = output capacitance to ground of the second-stage



$$-g_{mI}V_{in} = [G_I + s(C_I + C_c)]V_2 - [sC_c]V_{out}$$

$$0 = [g_{mII} - sC_c]V_2 + [G_{II} + sC_{II} + sC_c]V_{out}$$

$$\begin{aligned} \Rightarrow \frac{V_{out}(s)}{V_{in}(s)} &= \frac{g_{mI}(g_{mII} - sC_c)}{G_I G_{II} + s[G_{II}(C_I + C_{II}) + G_I(C_{II} + C_c) + g_{mII}C_c] + s^2[C_I C_{II} + C_c C_I + C_c C_{II}]} \\ &= \frac{A_o[1 - s(C_c/g_{mII})]}{1 + s[R_I(C_I + C_{II}) + R_{II}(C_2 + C_c) + g_{mII}R_I R_{II}C_c] + s^2[R_I R_{II}(C_I C_{II} + C_c C_I + C_c C_{II})]} \end{aligned}$$

where, $A_o = g_{mI}g_{mII}R_I R_{II}$



2-stage Op Amps with C_c

In general, $D(s) = \left(1 - \frac{s}{p_1}\right) \left(1 - \frac{s}{p_2}\right) = 1 - s \left(\frac{1}{p_1} + \frac{1}{p_2}\right) + \frac{s^2}{p_1 p_2} \rightarrow D(s) \approx 1 - \frac{s}{p_1} + \frac{s^2}{p_1 p_2}$, if $|p_2| \gg |p_1|$

$$p_1 = \frac{-1}{R_I(C_I + C_{II}) + R_{II}(C_{II} + C_c) + g_{mII} R_I R_{II} C_c} \approx \frac{-1}{g_{mII} R_I R_{II} C_c}$$

- Dominant left-half pole (the Miller pole)
- This root accomplishes the desired compensation

$$p_2 = \frac{-[R_I(C_I + C_{II}) + R_{II}(C_{II} + C_c) + g_{mII} R_I R_{II} C_c]}{R_I R_{II} (C_I C_{II} + C_c C_I + C_c C_{II})} \approx \frac{-g_{mII} C_c}{C_I C_{II} + C_c C_I + C_c C_{II}} \approx \frac{-g_{mII}}{C_{II}}$$

- Left-half plane output pole
- This pole must be \geq unity-gain-bandwidth or PM will not be satisfied

$$z = \frac{g_{mII}}{C_c} \quad (C_{II} > C_c \gg C_I)$$


- Right-half plane zero
- This root is very undesirable: it boosts the magnitude while decreasing the phase

Conceptually, where do these roots come from?




1) The Miller pole

$$|p_1| \approx \frac{1}{R_I (g_{m6} R_{II} C_c)}$$

 


2) The left-half plane output pole:

$$|p_2| \approx \frac{g_{m6}}{C_{II}}$$

 

 
3) Right-half plane zero (One source of zeros is from multiple paths from the input to output):

$$v_{out} = \left(\frac{-g_{m6} R_{II} \left(\frac{1}{sC_c} \right)}{R_{II} + \frac{1}{sC_c}} \right) V' + \left(\frac{R_{II}}{R_{II} + \frac{1}{sC_c}} \right) V'' = \frac{-R_{II} \left(\frac{g_{m6}}{sC_c} - 1 \right)}{R_{II} + \frac{1}{sC_c}} V$$



 4) Mirror pole-zero

$$p_3 = -\left(\frac{g_{m3}}{C_3} \right) \quad z_3 = -\left(\frac{2g_{m3}}{C_3} \right)$$





Outline

- ☐ General Consideration
- ☐ One-Stage Op Amps
- ☐ Two-Stage Op Amps
- ☐ Compensation of 2-Stage Op Amps
- ☐ Other Issues of Op Amps

Input Range Limitations

- Input common-mode level may need to vary over a wide range,

e.g. ADC input comparator.

- Input swing limits the total range sometimes.

Assume $V_{GS} \approx 0.9V$, $V_{DSsat} \approx 0.2V$, $V_{DD} = 1.5V$

- Input common-mode range **ICMR=0.9V**

$$V_{icm}(upper) = V_{DD} - V_{SD3}(sat) + V_{T1} \quad \text{2.0V}$$

$$V_{icm}(lower) = V_{DS5}(sat) + V_{GS1} \quad \text{1.1V}$$

- Minimum power supply (ICMR=0)

$$\begin{aligned} V_{DD}(\min) &= V_{SD3}(sat) - V_{T1} + V_{GS1} + V_{DS5}(sat) \\ &= V_{SD3}(sat) + V_{DS1}(sat) + V_{DS5}(sat) \end{aligned}$$

$$\text{0.6V}$$




Input pair: PMOS

Input Range Limitations


□ N-MOSTs differential pair

□ P-MOSTs differential pair

 


□ *How to extending the input CM range?*

-- Parallel Input Stage

 

Rail to rail Folded Cascode

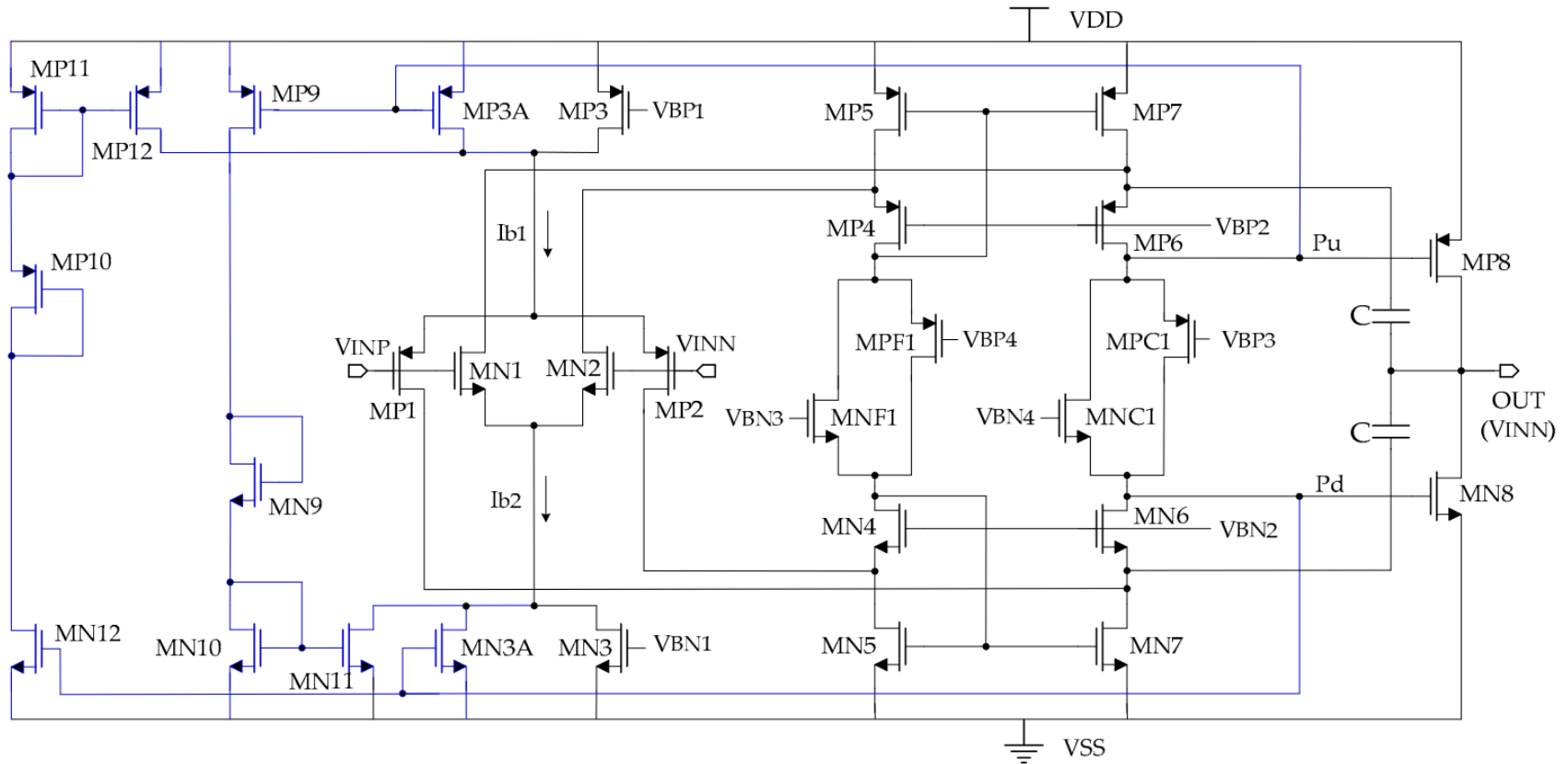

- Input Stage, Gain Stage, Output Stage
- + Bias Circuit, Frequency Compensation

Slew Rate


□ Concept of Slew Rate

□ Linear circuit

$$\frac{V_{out}}{V_{in}} = \frac{1/sC}{R + 1/sC} = \frac{1}{1 + sRC}$$

for an input step
 
$$V_{out} = V_0 \left[1 - \exp\left(\frac{-t}{\tau}\right) \right] \quad \frac{dV_{out}}{dt} = \frac{V_0}{\tau} \exp\left(\frac{-t}{\tau}\right)$$




□ the slope of the step response is proportional to the final output value V_0

□ Linear feedback system with op amp

$$\beta = \frac{R_2}{R_1 + R_2}$$
 
$$V_{out} = \frac{AV_0}{1 + A\beta} \left[1 - \exp\left(\frac{-t}{C_L R_{out} / (1 + A\beta)}\right) \right] u(t)$$




Linear feedback system with real op amp



- ❑ With large input steps, the output displays a linear ramp having a constant slope. The slope of ramp is the “**slew rate**”.
- ❑ It seems that **the maximum current to charge** the load capacitance is limited.
- ❑ Nonlinear behaviors **reduce speed** and increase distortion.
- ❑ Increase SR would consume power and wider device

Trade off
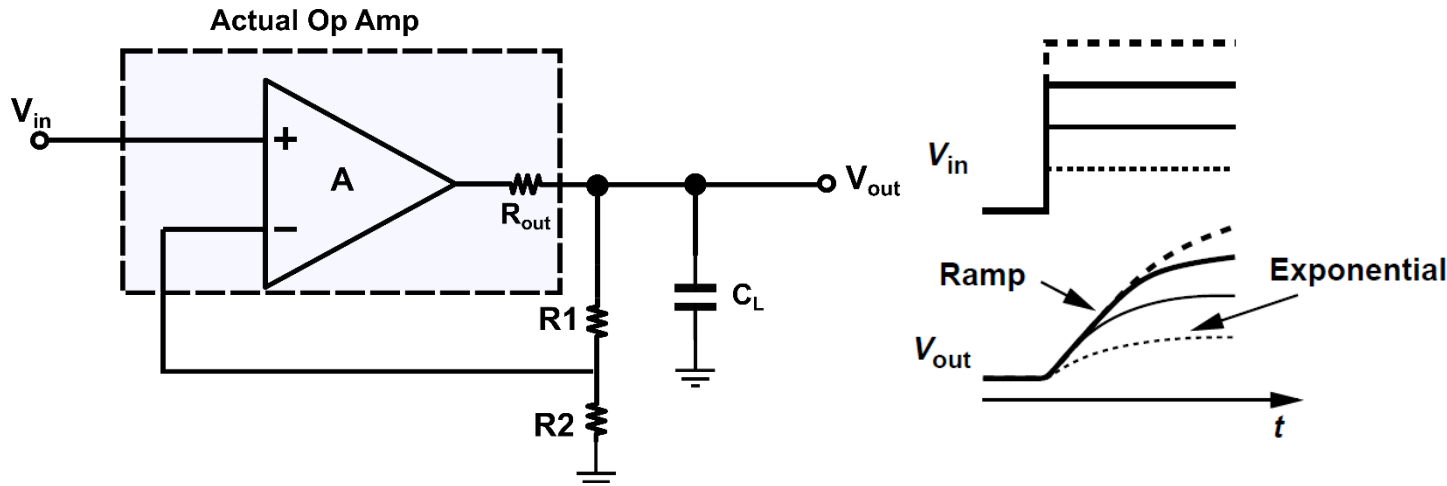
$$I = C_L \frac{dV_{out}}{dt} = \frac{AV_0}{R_{out}} \exp \left[\frac{-(1 + A\beta)t}{R_{out}C_L} \right]$$



Slewing in op amp


□ $V_{in} : \uparrow \Delta V,$

$$V_{G1} \uparrow : I_{D1} \uparrow \quad g_m \Delta V / 2$$

$$V_{G2} \downarrow : I_{D2} \downarrow \quad g_m \Delta V / 2$$

=> the charging current to C_L :

$$I = g_m \Delta V$$

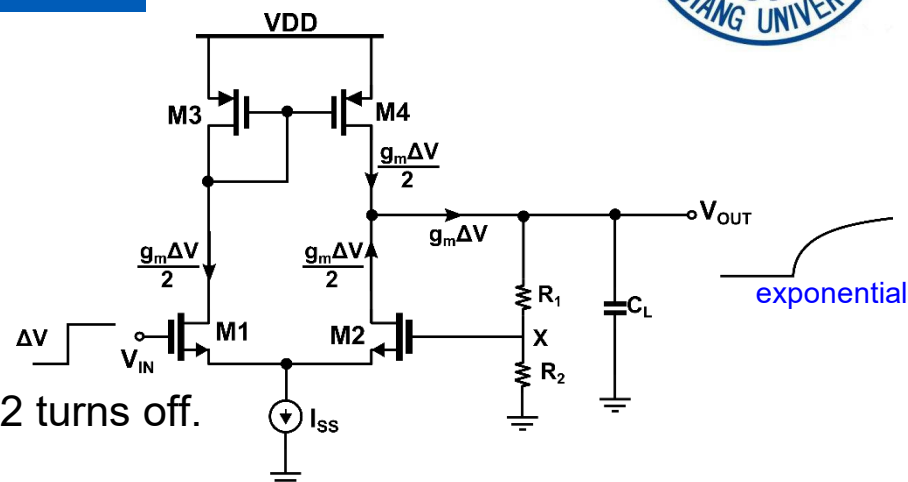

□ When M1 experiences a large step, M2 turns off.

□ C_L : a constant current $I_{SS} = g_m \Delta V$

□ Feedback is broken but after M2 turns on,

□ the circuit returns to a linear operation.

□ Slew rate:


$$I_{SS} / C_L$$

be independent of the input !!!

□ $V_{in} \downarrow \Delta V$

-- Slew rate:

$$I_{SS} / C_L$$

 


Slew Rate of Telescopic and Folded op amp





Telescopic op amp

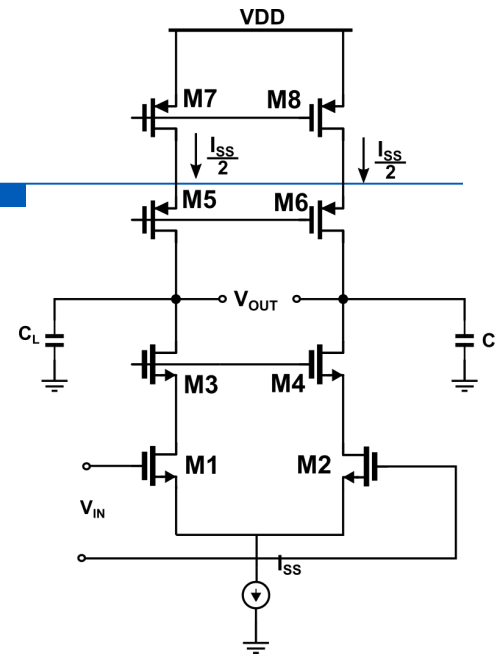- The ramp slope in each side: $\pm I_{SS} / (2C_L)$
- The slew rate for $V_{out1} - V_{out2}$: I_{SS} / C_L




Folded op amp

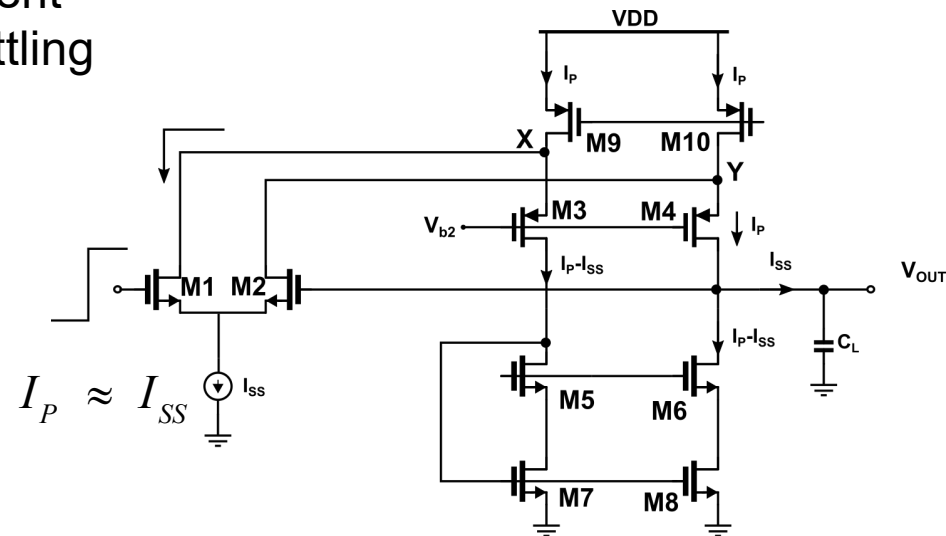 - if $I_P \geq I_{SS}$, slew rate: I_{SS} / C_L
- if $I_{SS} > I_P$, M3 turns off and tail current source enters the triode region. The settling time increases.




Other examples (1)

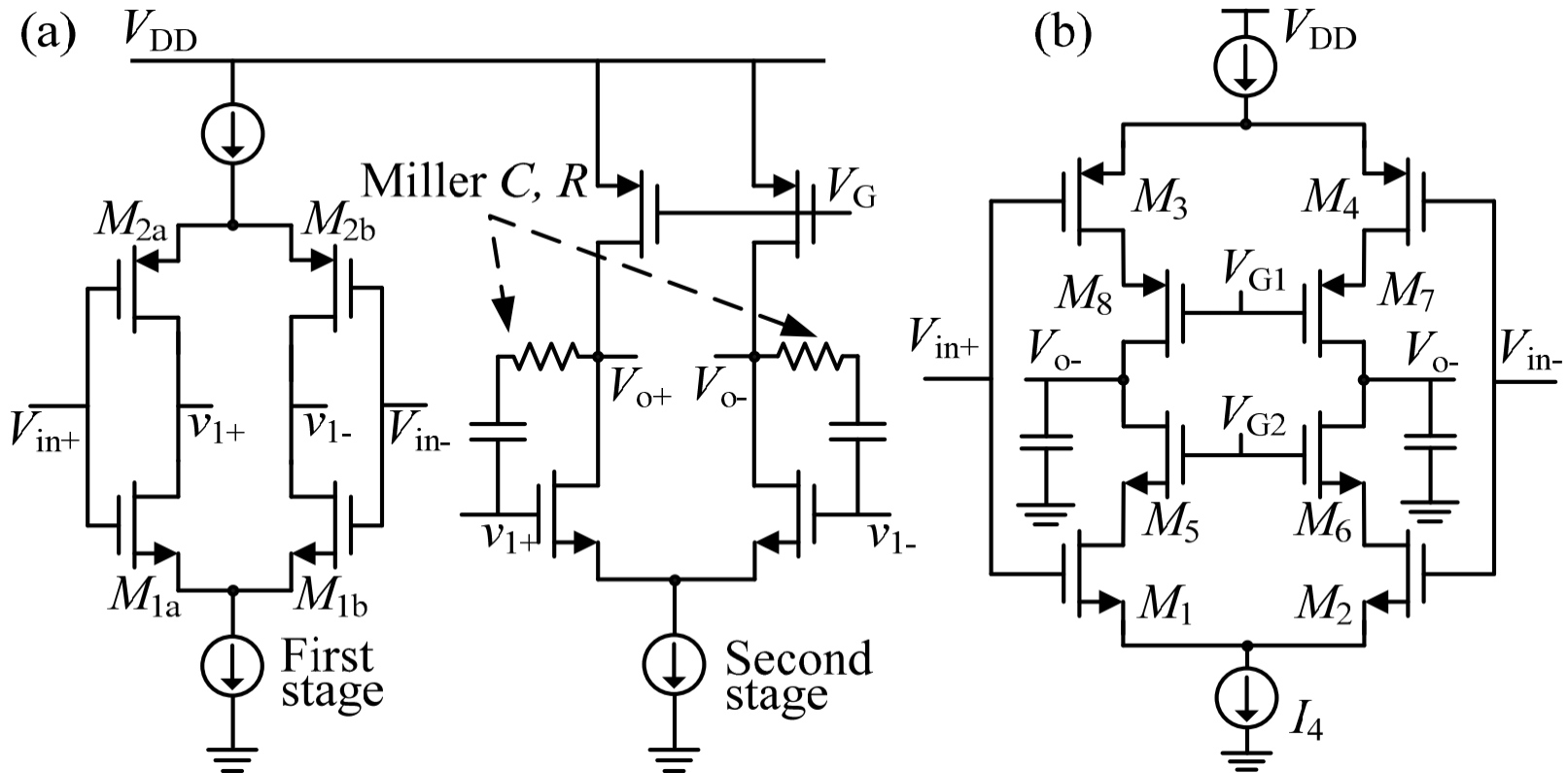

- Current reuse: two stage and telescopic

Other examples (2)

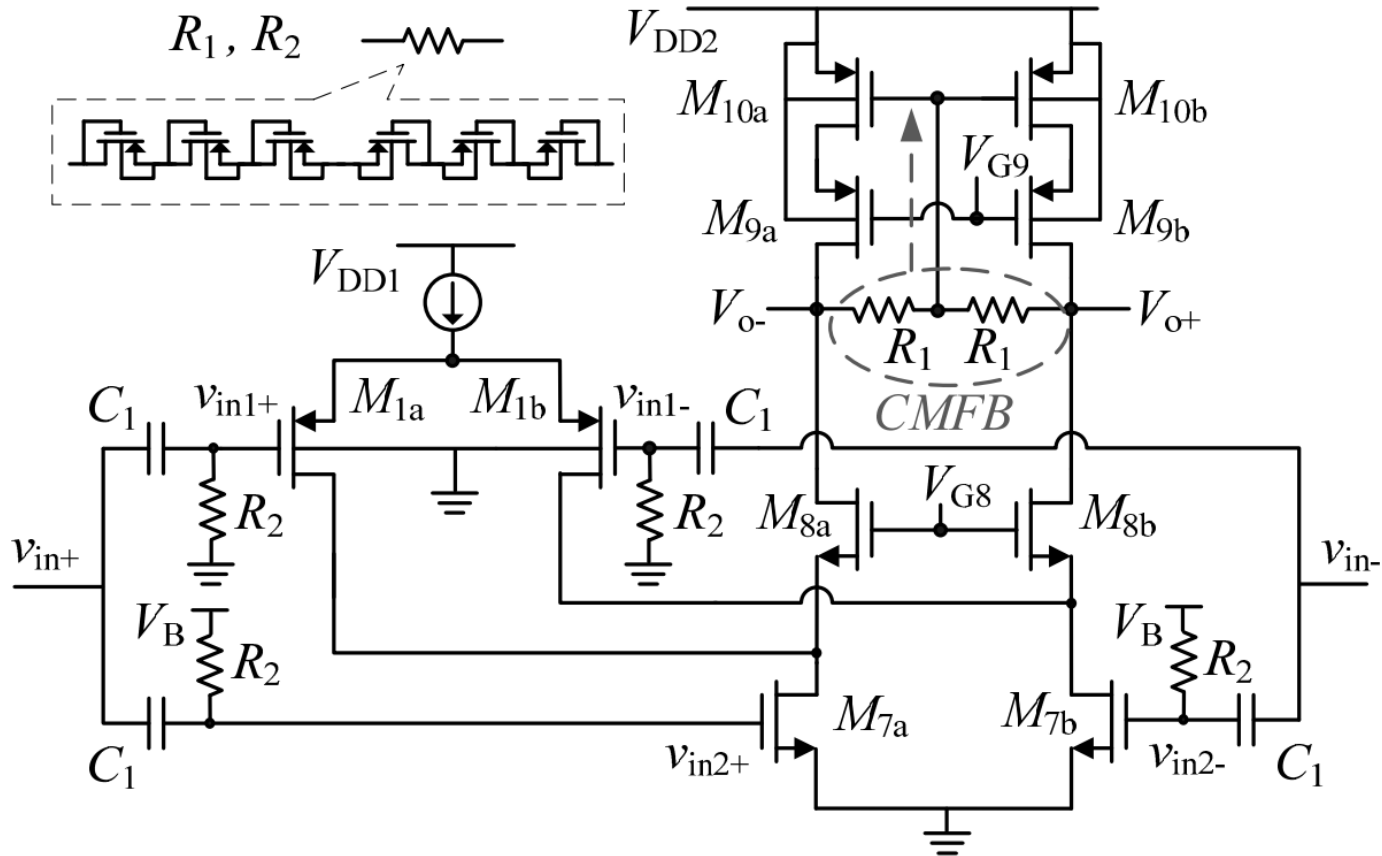

- Current reuse: folded cascode

Summary

- ❑ Ideal Opamp
- ❑ DC gain and dominant pole of single stage, telescopic and folded-cascade amplifier
- ❑ DC gain and two poles of two stage amplifier, after miller compensation
- ❑ Input and output range
(everyone in saturation)
- ❑ Speed and Slew rate
(small signal and large signal behavior)



集成电路原理与设计

10. 运算放大器

宋爽

shuangsonghz@zju.edu.cn