



| Parameter Symbol | Parameter Description                      | Typical Parameter Value                                  |  | Units                    |
|------------------|--|--|--|--------------------------|
|                  |  | n-Channel  | p-Channel  |                          |
| $V_{T0}$         | Threshold voltage ( $V_{BS} = 0$ )         | $0.7 \pm 0.15$   | $-0.7 \pm 0.15$  | V                        |
| $K'$             | Transconductance parameter (in saturation) | $110.0 \pm 10\%$   | $50.0 \pm 10\%$  | $\mu\text{A}/\text{V}^2$ |
| $\gamma$         | Bulk threshold parameter                   | 0.4  | 0.57   | $\text{V}^{1/2}$         |
| $\lambda$        | Channel length modulation parameter        | $0.04 (L = 1 \mu\text{m})$<br>$0.01 (L = 2 \mu\text{m})$ | $0.05 (L = 1 \mu\text{m})$<br>$0.01 (L = 2 \mu\text{m})$ | $\text{V}^{-1}$          |
| $2 \phi_F $      | Surface potential at strong inversion      | 0.7  | 0.8  | V                        |

$$\frac{\partial V_{ref}}{\partial T} = L \cdot \ln K \cdot \frac{\partial V_T}{\partial T} + \frac{\partial V_{d3}}{\partial T} = 0$$

It can be derived that while  $L \ln K = 2/0.085 = 23.5$ ,  $\frac{\partial V_{ref}}{\partial T} = 0$ , or  $TC(V_{ref}) = 0$ .

Assuming  $K=10$ , the corresponding  $L = 10.2 \approx 10$

Under these conditions the  $V_{ref}$  that has zero TC is

$$V_{REF} = L \ln K \times V_T + V_{BE(D3)} = 1.35V$$

5.2 Derive an expression for  $I_{out}$  in Fig 5.2. Assume all transistors are in saturation region, and  $(W/L)_4 = (W/L)_3$ ,  $\lambda = 0$ .

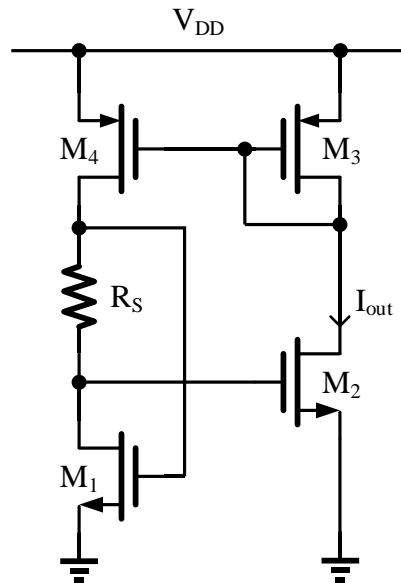


Fig 5.2

解:

$$I_{out} R_S + \sqrt{\frac{2I_{out}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_2}} + V_{TH2} = \sqrt{\frac{2I_{out}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}} + V_{TH1}$$

$$\text{解得: } I_{out} = \frac{2}{\mu_n C_{ox} R_S^2} \left( \sqrt{\left(\frac{L}{W}\right)_1} - \sqrt{\left(\frac{L}{W}\right)_2} \right)^2$$

5.3 The circuit of Fig 5.3 is designed with  $R_3 = 1k\Omega$ , and a current of  $50\mu A$  through it. Calculate  $R_1$  and  $n$  for a zero TC. Assume  $R_1 = R_2$ . Assume  $(\partial V_T)/\partial T = 0.085mV/^\circ C$ ,  $(\partial V_{BE2})/\partial T = -2mV/^\circ C$ ,  $V_{BE} = 0.75V$ ,  $V_T = 26mV$ .

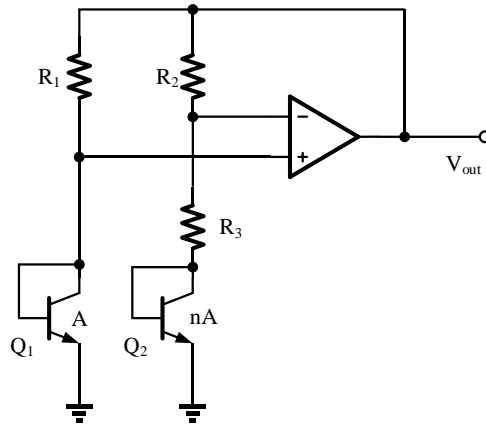


Fig 5.3

解：

$$V_{out} = V_{BE2} + (V_T \ln n) \left( 1 + \frac{R_2}{R_3} \right)$$

$$I_{R3} = \frac{V_{out} - V_{BE2}}{R_2 + R_3} = \frac{(V_T \ln n) \left( 1 + \frac{R_2}{R_3} \right)}{R_2 + R_3} = 50 \mu A$$

$$\frac{\partial V_{out}}{\partial T} = \frac{\partial V_{BE}}{\partial T} + \left( 1 + \frac{R_2}{R_3} \right) \ln n \times \frac{\partial V_T}{\partial T} = 0$$

解得：  $R_2 = 11.2 k\Omega$  ,  $n \approx 6.84$