



# 集成电路原理与设计

## 11. 反相器

宋爽

shuangsonghz@zju.edu.cn

# Syllabus

课数	内容	课数	内容
1	导论	9	差分放大器
2	器件模型	10	运算放大器
3	电容特性, 小信号模型	11	导线
4	工艺流程	12	反相器
5	模拟基本单元	13	组合逻辑
6	电流镜与基准	14	时序逻辑
7	单级放大器	15	集成电路专题讲座一
8	课堂测验	16	集成电路专题讲座二

# Goals

---

- ❑ Quantification of integrity, performance and energy metrics of an inverter
- ❑ Optimization of an inverter design (**delay optimization**)

## ***Design metrics of the gate***

- ❑ ***Cost:*** complexity, area
- ❑ ***Integrity and robustness:*** static (or steady-state) behavior
- ❑ ***Performance:*** dynamic (or transient) response
- ❑ ***Energy efficiency:*** energy and power consumption

# Outline

---



- **Inverter Basic Characteristics**
- **Static Behavior**
- **Dynamic Behavior**
- **Power, Energy**

*Reference:*



*Chapter 5, <Digital Integrated Circuits: A design perspective> Rabaey 著*

---




# CMOS Inverter: A first glance

  


# Appendix: Two Inverters

  

# First-Order DC Analysis

  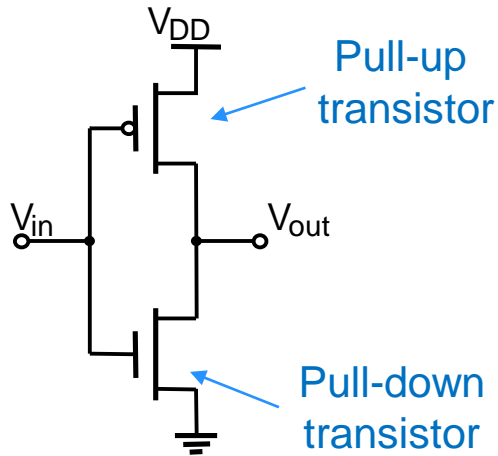

$$V_{in} = 0$$

 

$$\begin{aligned} V_{OL} &= 0 \\ V_{OH} &= V_{DD} \\ V_M &= f(R_n, R_p) \end{aligned}$$

$$V_{in} = V_{DD}$$


# First-Order DC Analysis: Properties

---

- Full **rail-to-rail** swing  $\Rightarrow$  **high noise margins**
- Logic levels not dependent upon the relative device sizes  
 $\Rightarrow$  transistors can be minimum size **ratioless** 无比电路
- Always a path between  $V_{\text{out}}$  to  $V_{\text{DD}}$  or GND in steady state  
 $\Rightarrow$  **low output impedance** ( $\sim k\Omega$ )  
 $\Rightarrow$  less sensitive to noise and disturbances
- Extremely high input resistance  
 $\Rightarrow$  nearly zero steady-state input current  
 $\Rightarrow$  **large fan-out** (albeit it with degraded performance: delay)
- No direct path in steady-state between power and ground  
 $\Rightarrow$  **no static power dissipation** (ignores leakage current)
- Propagation delay function of load capacitance and resistance of transistors



 
# Review: Short Channel I-V Plot (NMOS/PMOS)



NMOS transistor 0.25 $\mu$ m,  
 $L_d = 0.25\mu$ m,  $W/L = 1.5$ ,  
 $V_{DD} = 2.5V$ ,  $V_T = 0.4V$

 PMOS transistor 0.25 $\mu$ m,  
 $L_d = 0.25\mu$ m,  $W/L = 1.5$ ,  
 $V_{DD} = 2.5V$ ,  $V_T = -0.4V$






# Review: Transforming PMOS I-V Lines

- Want common coordinate set  $V_{in}$ ,  $V_{out}$ , and  $I_{Dn}$


$$I_{DSp} = -I_{DSn}$$

$$V_{GSn} = V_{in} ; V_{GSp} = V_{in} - V_{DD}$$
   
$$V_{DSn} = V_{out} ; V_{DSp} = V_{out} - V_{DD}$$




# CMOS Inverter Load Lines


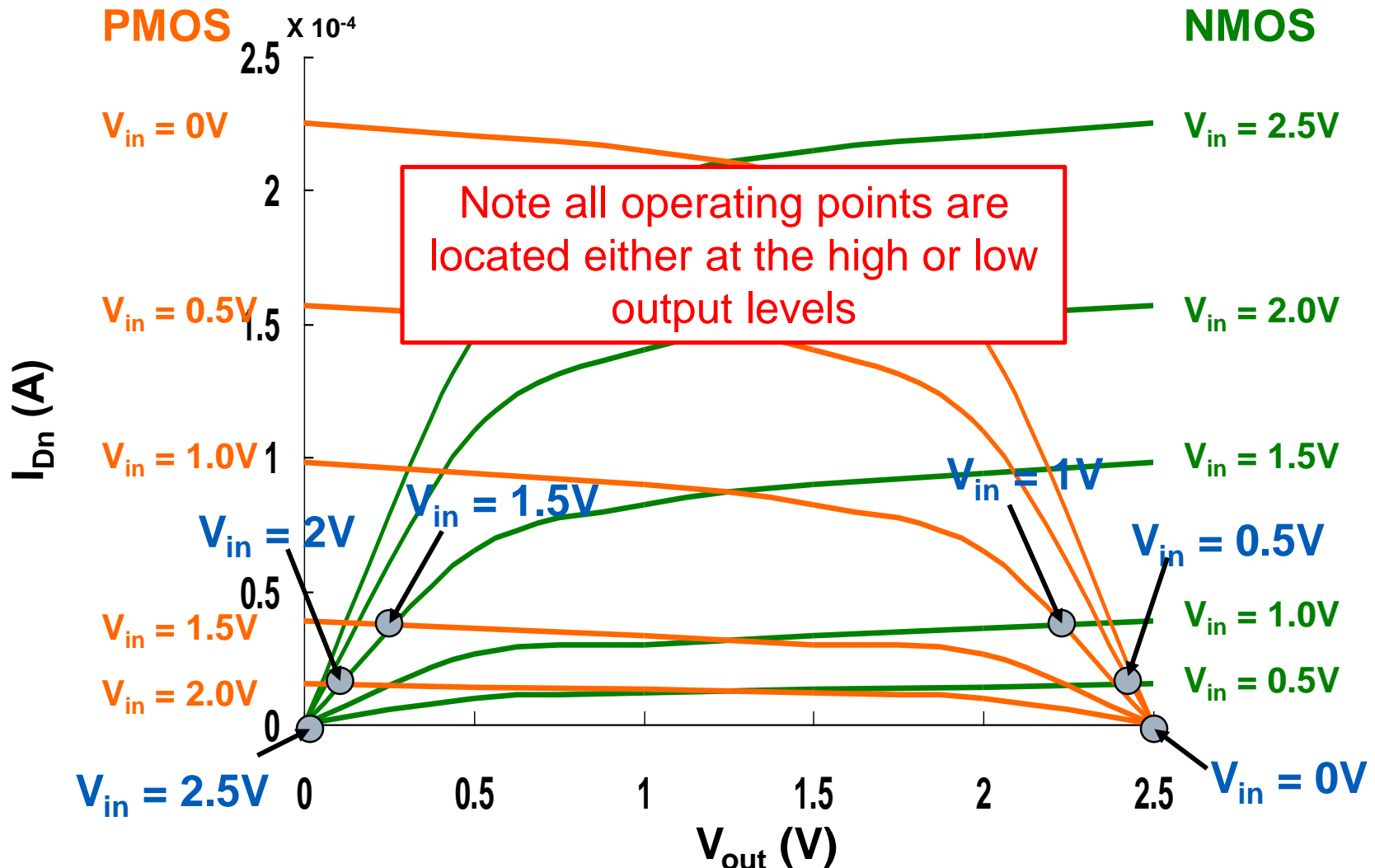


0.25um,  $W/L_n = 1.5$ ,  $W/L_p = 4.5$ ,  $V_{DD} = 2.5V$ ,  $V_{Tn} = 0.4V$ ,  $V_{Tp} = -0.4V$

# CMOS Inverter VTC

 

# Switch Model of Dynamic Behavior

  

Gate response time is determined by the time to

- charge  $C_L$  through  $R_p$
- discharge  $C_L$  through  $R_n$

**A fast gate is build either by keeping the output capacitance small and by decreasing the on-resistance of the transistor**

# Outline


## □ Inverter Basic Characteristics

## □ Static Behavior

- Switching Threshold
- Noise Margin
- Robustness Revisited

## □ Dynamic Behavior

## □ Power, Energy

 

# Switching Threshold



- $V_M$ :  $V_{in} = V_{out}$  (both PMOS and NMOS in saturation,  $V_{DS} = V_{GS}$ ) assumed to be velocity-saturated ( $V_{DSAT} < V_M - V_T$ ), and ignore the channel length modulation effects

$$k_n V_{DSATn} \left( V_M - V_{Tn} - \frac{V_{DSATn}}{2} \right) + k_p V_{DSATp} \left( V_M - V_{DD} - V_{Tp} - \frac{V_{DSATp}}{2} \right) = 0$$

Solving for  $V_M$  yields

$$V_M = \frac{\left( V_{Tn} + \frac{V_{DSATn}}{2} \right) + r \left( V_{DD} + V_{Tp} + \frac{V_{DSATp}}{2} \right)}{1 + r} \quad \text{with } r = \frac{k_p V_{DSATp}}{k_n V_{DSATn}} = \frac{v_{satp} W_p}{v_{satn} W_n}$$


$$V_M \approx r V_{DD} / (1 + r)$$



$r$ : the **relative driving strengths** of PMOS/NMOS

- $r$  set the switching threshold
- $r \approx 1$ :  $V_M = V_{DD}/2 \Rightarrow$  comparable high and low noise margins
- To move  $V_M$  upwards, a larger  $r$  is required making PMOS wider
- Increasing the strength of NMOS, moves  $V_M$  closer to GND

# Recall the Velocity Saturation

 


<b>Velocity Saturation</b>	$I_{DS} = v_{sat} W C_{ox} (V_{GS} - V_{TH})$
----------------------------	---

**Strong Inversion**

$$I_{DS} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

 **Weak Inversion**

$$I_{DS} = I_0 \exp \frac{V_{GS}}{n k T / q}$$





# Switching Threshold: $r$

$$V_M \approx rV_{DD} / (1 + r) \quad \text{where } r = k_p V_{DSATp} / k_n V_{DSATn}$$

## Example

In generic 0.25 $\mu$ m CMOS process,  $V_{DD} = 2.5V$ , and a minimum size NMOS device:  $(W/L)_n = 1.5$

	$V_{T0}(V)$	$\gamma(V^{0.5})$	$V_{DSAT}(V)$	$k'(A/V^2)$	$\lambda(V^{-1})$
NMOS	0.43	0.4	0.63	$115 \times 10^{-6}$	0.06
PMOS	-0.4	-0.4	-1	$-30 \times 10^{-6}$	-0.1

$$\frac{(W/L)_p}{(W/L)_n} = \frac{115 \times 10^{-6} \times 0.63 \times (1.25 - 0.43 - 0.63/2)}{30 \times 10^{-6} \times 1.0 \times (1.25 - 0.4 + 1.0/2)} = 3.5 \Rightarrow (W/L)_p = 3.5 \times 1.5 = 5.25$$




Velocity saturation does not occur:

$$V_M = \frac{V_{Tn} + r(V_{DD} + V_{Tp})}{1 + r} \quad \text{with } r = \sqrt{\frac{-k_p}{k_n}}$$



When designing static CMOS circuits, to balance the driving strengths of the transistors by **making PMOS wider than NMOS**, if one wants to maximize the noise margins and obtain symmetrical characteristics

# Simulated Inverter $V_M$

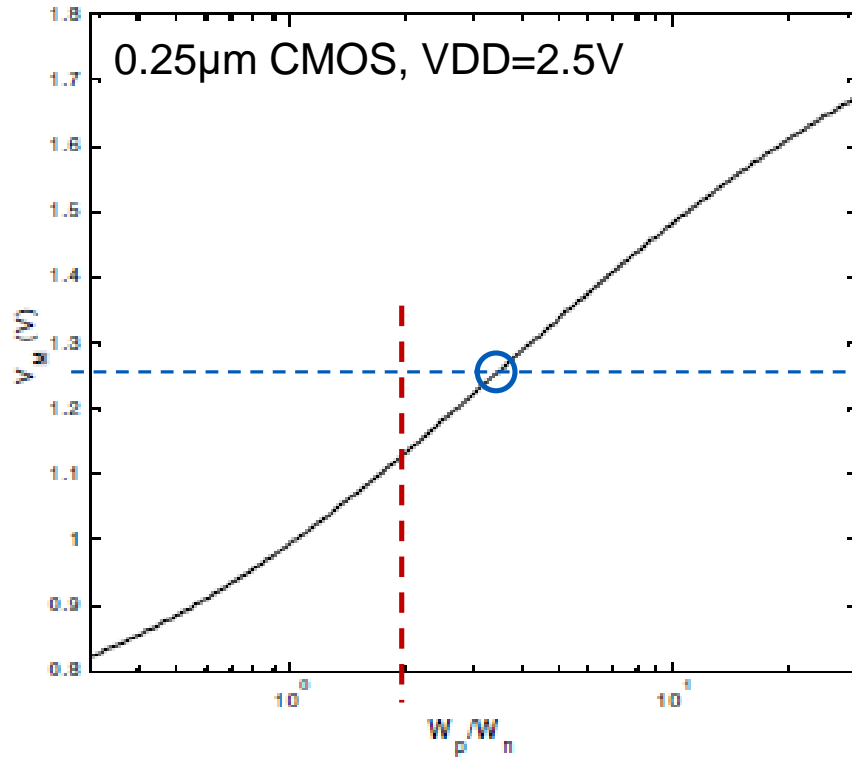


- $V_M$  is relatively insensitive to variations in device ratio

$r$	3.4	3	2.5	2
$V_M$	1.25	1.22	1.18	1.13

- $r$ : shift the transient region of VTC
  - Increasing  $W_p$  moves  $V_M$  towards VDD
  - Increasing  $W_n$  moves  $V_M$  towards GND

*inverter with asymmetrical  $V_M$*

# Noise Margins

 

A simplified approach

$$V_{IH}, V_{IL}: \frac{dV_{out}}{dV_{in}} = -1$$

$$V_{IH} - V_{IL} = -\frac{V_{OH} - V_{OL}}{g} = -\frac{V_{DD}}{g}$$

$$V_{IH} = V_M - \frac{V_M}{g}$$

$$V_{IL} = V_M + \frac{V_{DD} - V_M}{g}$$

$$NM_H = V_{DD} - V_{IH} \quad NM_L = V_{IL}$$


⇒ a high gain in transition region

$$V_M: g \approx \frac{1+r}{(V_M - V_{Tn} - V_{DSATn}/2)(\lambda_n - \lambda_p)}$$



?  $g \rightarrow \infty$

$$NM_H = V_{OH} - V_M$$

$$NM_L = V_M - V_{OL}$$

 

# Inverter Gain

  


$$g = -\frac{1}{I_D(V_M)} \frac{k_n V_{DSATn} + k_p V_{DSATp}}{\lambda_n - \lambda_p} \approx \frac{1+r}{(V_M - V_{Tn} - V_{DSATn}/2)(\lambda_n - \lambda_p)}$$



**Analog IC vs. Digital IC**

# Impact of Process Variations

 

## A good device:


a small oxide thickness (-3nm),  
a small length (-25nm),  
a higher width (+30nm)  
a smaller threshold (-60mV).

## A bad device: the opposite


⇒ a shift in  $V_M$

**Corner model**

# Gain as a function of $V_{DD}$

 

$$V_{TH} = \pm 0.4V$$

 

$$V_{DD\min} > (2 \sim 4) \frac{kT}{q} \quad \phi_T = \frac{kT}{q} = 26mV (300K)$$





# Outline

---

- ☐ Inverter Basic Characteristics
- ☐ Static Behavior
- ☐ **Dynamic Behavior**
  - **Propagation delay: first-order analysis**
  - Propagation delay from perspective
- ☐ Power, Energy

# $C_L$ in CMOS Inverters

 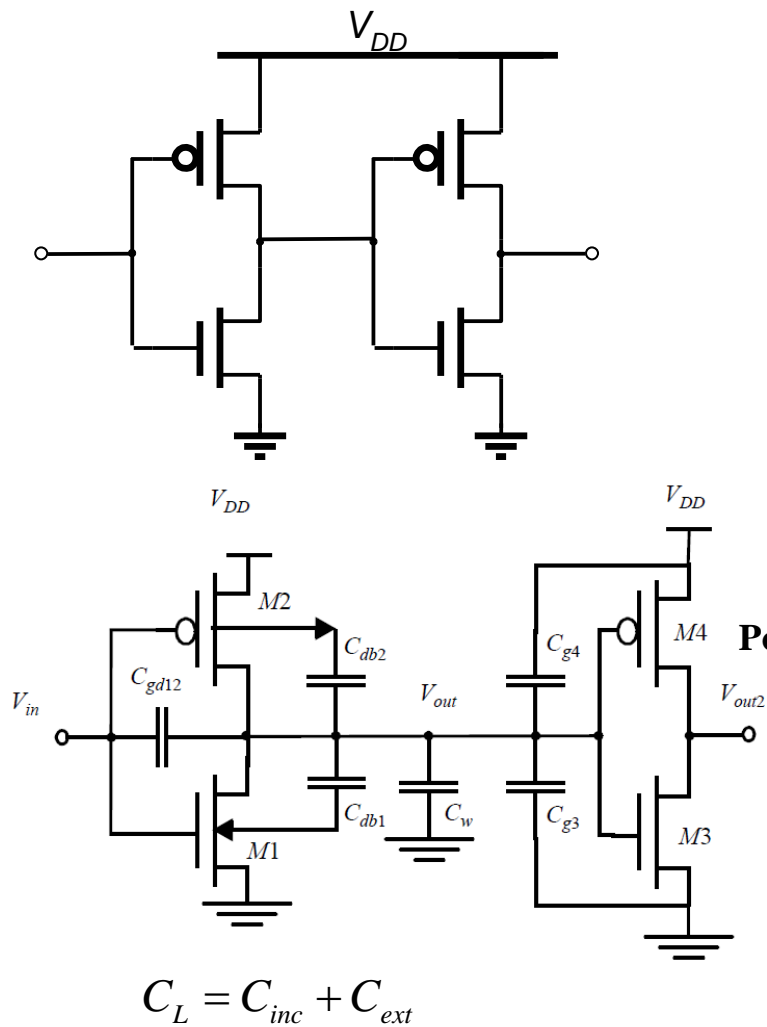



# Inverter Propagation Delay

- Propagation delay is proportional to the time-constant of the network formed by the pull-down resistor and the load capacitance


$$t_p = \int_{v_1}^{v_2} \frac{C_L(v)}{i(v)} dv = f(R_n, C_L)$$

**first-order linear RC-network:**

$$t_{pHL} = \ln(2) R_{eqn} C_L = 0.69 R_{eqn} C_L$$

$$t_{pLH} = \ln(2) R_{eqp} C_L = 0.69 R_{eqp} C_L$$

 
$$t_p = (t_{pHL} + t_{pLH}) / 2 = 0.69 C_L (R_{eqn} + R_{eqp}) / 2$$



$$\Rightarrow t_{pHL} = t_{pLH} \quad R_{eqn} = R_{eqp}$$

**a symmetrical VTC**

## Appendix : Equivalent Resistance

 


$$R_{eq} = \frac{1}{-V_{DD}/2} \int_{V_{DD}}^{V_{DD}/2} \frac{V}{I_{DSAT}(1+\lambda V)} dV \approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left(1 - \frac{7}{9} \lambda V_{DD}\right)$$

$$R_{eq} = \frac{1}{2} \left( \frac{V_{DD}}{I_{DSAT}(1+\lambda V_{DD})} + \frac{V_{DD}/2}{I_{DSAT}(1+\lambda V_{DD}/2)} \right) \approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left(1 - \frac{5}{6} \lambda V_{DD}\right)$$


$$I_{DSAT} = k' \frac{W}{L} \left( (V_{DD} - V_T) V_{DSAT} - \frac{V_{DSAT}^2}{2} \right)$$

# Transient Response

 
 
# Delay as a function of VDD

? How to manipulate or optimize the delay?



# Design for Propagation Delay

---

- **Reduce  $C_L$** 
  - internal diffusion capacitance of the gate itself
    - ⇒ *keep the drain diffusion as small as possible*
  - interconnect capacitance
  - Fanout capacitance
- **Increase W/L ratio** of the transistor
  - the most powerful and effective performance optimization tool in the hands of the designer*
  - **self-loading!**  $C_{inc} > C_{ext}$
- **Increase  $V_{DD}$** 
  - trade-off: **energy** vs. **performance**
  - increasing  $V_{DD}$  above a certain level yields only very minimal improvements
  - reliability: oxide breakdown, hot-electron effects






# Outline

---

- Inverter Basic Characteristics
- Static Behavior
- **Dynamic Behavior**
  - Propagation Delay: First-order Analysis
  - **Propagation Delay from Perspective**
    - ✓ NMOS/PMOS Ratio
    - ✓ Sizing Inverters for Performance
    - ✓ Sizing a Chain of Inverters and its Stage
    - ✓ Rise/fall Time of Input Signal
    - ✓ Delay in Long Interconnect Wires
 
# NMOS/PMOS Ratio

- Symmetrical VT and  $t_{pHL} = t_{pLH}$ :  $\beta = (W/L_p)/(W/L_n) = 3 \sim 3.5$
- If speed is the only concern, **reduce** the width of the PMOS device



$$t_p = (t_{pHL} + t_{pLH})/2$$

widening PMOS degrades  $t_{pHL}$   
due to larger parasitic  
capacitance

$$\frac{\partial t_p}{\partial \beta} = 0 \Rightarrow \beta_{opt} = \sqrt{\gamma \left(1 + \frac{C_w}{C_{dn1} + C_{gn2}}\right)}$$

- $\beta$  of 2.4 (= 31 k $\Omega$ /13 k $\Omega$ ):  
symmetrical response
- $\beta$  of 1.6 to 1.9:  
optimal performance

# Device Sizing for Performance

- Divide capacitive load,  $C_L$ , into  $C_L = C_{int} + C_{ext}$ 
  - $C_{int}$ : intrinsic (self-loading) cap - diffusion and gate-drain (Miller) effect
  - $C_{ext}$ : extrinsic load cap- wiring and fanout

$$t_p = 0.69 R_{eq} C_{int} (1 + C_{ext}/C_{int}) = t_{p0} (1 + C_{ext}/C_{int})$$

- **intrinsic delay** (unloaded,  $C_{ext}=0$ )

$$t_{p0} = 0.69 R_{eq} C_{int}$$


- Size factor:  $S$  (reference gate)

$$C_{int} = S C_{iref}$$

$$\begin{aligned} t_p &= 0.69 R_{eq} C_{int} (1 + C_{ext}/C_{int}) \\ &= t_{p0} (1 + C_{ext}/S C_{iref}) \end{aligned}$$

--  $t_{p0}$  : the size of gate **X**  
 technology and layout **✓**

--  $S \uparrow, t_p \rightarrow t_{p0}$

 




# Impact of Fanout on Delay

---

- $C_{\text{ext}}$ : a function of the fanout of the gate  
*The larger the fanout, the larger the external load.*
- Determine the input loading effect of the inverter.
  - Both  $C_g$  and  $C_{\text{int}}$  are proportional to the **gate sizing**  $C_{\text{int}} = \gamma C_g$   
$$t_p = t_{p0} (1 + C_{\text{ext}} / \gamma C_g) = t_{p0} (1 + \textcircled{f/\gamma})$$
  
the effective fan-out:  $\mathbf{f} = \mathbf{C_{\text{ext}}/C_g}$
- The delay of an inverter is a function of  $f$
 
# Apply to Inverter Chain

- Goal: minimize the delay through an inverter chain



The delay of the  $j$ -th inverter stage:

$$t_{p,j} = t_{p0} (1 + C_{g,j+1} / (\gamma C_{g,j})) = t_{p0} (1 + f_j / \gamma)$$

and  $t_p = t_{p1} + t_{p2} + \dots + t_{pN} \Rightarrow t_p = \sum t_{p,j} = t_{p0} \sum (1 + C_{g,j+1} / (\gamma C_{g,j}))$

$$\frac{\partial t_p}{\partial C_{g,j}} = 0 \Rightarrow C_{g,j+1} / C_{g,j} = C_{g,j} / C_{g,j-1}$$

$$C_{g,j} = \sqrt{C_{g,j-1} C_{g,j+1}}$$



- The optimum size of each inverter is the **geometric mean of its neighbors sizes.**

# Apply to Inverter Chain


- The optimum size of each inverter will have the same effective fan-out and the same delay  $f = \sqrt[N]{C_L/C_{g,1}} = \sqrt[N]{F}$

$F$ : the overall effective fan-out of the circuit ( $F = C_L/C_{g,1}$ )

- The minimum delay through the inverter chain is

$$t_p = N t_{p0} \left( 1 + \sqrt[N]{F} / \gamma \right)$$

## Example

 

$C_L/C_1$  has to be evenly distributed across  $N = 3$  stages:  $f = \sqrt[3]{8} = 2$

# Optimum Stages $N$ in Inverter Chain


---

- What is the optimal value for  $N$  given  $F (=f^N)$  ?

$$t_p = Nt_{p0} \left( 1 + \sqrt[N]{F} / \gamma \right) \qquad f = \exp(1 + \gamma / f)$$


- if  $N$  is too large, the **intrinsic delay** of the stages becomes dominate
- if  $N$  is too small, the **effective fan-out** of each stage becomes dominate
- The optimal number of stages:  **$N = \ln(F)$**   
the effective fanout of each stage  $f = 2.71828 = e$

# Optimum Effective Fan-Out

 

- ❑ Choosing  $f$  larger than optimum has little effect on delay and reduces the number of stages (and area).
  - ❑ **Common practice to use:  $f = 4$  (for  $\gamma = 1$ )**
  - ❑ But **too many** stages has a substantial negative impact on delay

## Example: Inverter (Buffer) Staging

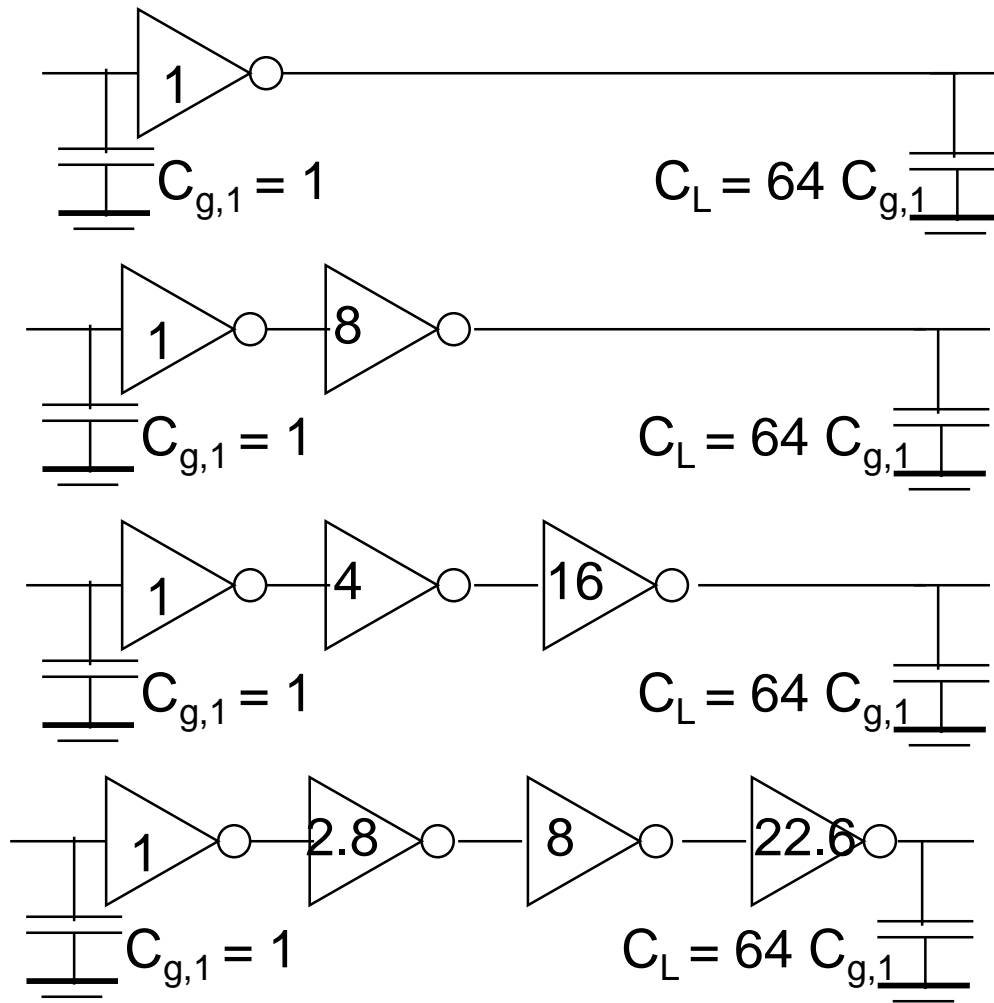

$$t_p = N * t_{p0}(1 + f_j / \gamma)$$

N	f	$t_p$
1	64	65
2	8	18
3	4	15
4	2.8	15.2

$$f = \sqrt[N]{F}$$

## Example: Impact of Buffer Staging

$t_{p,opt}/t_{p0}$	<b>F (<math>\gamma = 1</math>)</b>	<b>Unbuffered</b>	<b>Two Stage Chain</b>	<b>Opt. Inverter Chain</b>
	10	11	8.3	8.3
	100	101	22	16.5
	1,000	1001	65	24.8
	10,000	10,001	202	33.1

$$t_p = Nt_{p0} \left( 1 + \sqrt[N]{F} / \gamma \right)$$




When driving very large  $C_L$ , the impressive speed-up obtained with cascaded inverters.
 
# Input Signal Rise/Fall Time

- In reality, the input signal changes gradually (and both PMOS and NMOS conduct for a brief time). This affects the current available for charging/discharging  $C_L$  and impacts propagation delay.
- $t_p$  increases linearly with increasing input slope,  $t_s$ , once  $t_s > t_p$
- $t_s$  is due to the limited driving capability of the preceding gate

$$t_p^i = t_{step}^i + \eta t_{step}^{i-1}$$



for a minimum-size inverter with a fan-out of a single gate




# Design Challenge

---

- Keep signal rise times smaller than or equal to the gate propagation delays.
  - Good for performance
  - Good for power consumption
- Keep rise and fall times of the signals small and of approximately equal values is one of the major challenges in high-performance designs - slope engineering.
 
# Delay with Long Interconnects

- When gates are farther apart, wire capacitance and resistance can no longer be ignored.



$$t_p = 0.69R_{dr}C_{int} + (0.69R_{dr} + 0.38R_w)C_w + 0.69(R_{dr} + R_w)C_{fan}$$

$$= 0.69R_{dr}(C_{int} + C_{fan}) + 0.69(R_{dr}c_w + r_wC_{fan})L + 0.38r_wc_wL^2$$

$$\text{where } R_{dr} = (R_{eqn} + R_{eqp})/2$$

Wire delay rapidly becomes the dominate factor (due to the quadratic term) in the delay budget for longer wires.

**Add buffer per > 200μm wire**



# Outline

---


- Inverter Basic Characteristics
- Static Behavior
- Dynamic Behavior
- **Power, Energy**
  - **Dynamic Power Consumption**
  - **Static Consumption**

# Where Does Power Go?

---

- Dynamic Power:  $P_{\text{dynamic}} = P_{\text{switching}} + P_{\text{shortcircuit}}$ 
  - Charging and Discharging Capacitors
  - Short Circuit Currents: Short Circuit Path between Supply Rails during Switching
- Static Power:  $P_{\text{static}} = (I_{\text{sub}} + I_{\text{junct}} + I_{\text{gate}}) V_{\text{DD}}$ 
  - Leakage Static Consumption: OFF devices
    - Subthreshold Leakage
    - Junction Leakage
    - Gate Leakage

# Dynamic Power Consumption

 

## □ When the gate output rises

$$E_{VDD} = \int_0^{\infty} i_{VDD} V_{DD} dt = \dots = C_L V_{DD}^2$$

taken from the supply during the transition.

$$E_C = \int_0^{\infty} i_{VDD} V_{out} dt = \dots = C_L V_{DD}^2 / 2$$

stored on the capacitor at the end of the transition


Half the energy from  $V_{DD}$  is dissipated in the PMOS transistor as heat, other half stored in capacitor

## □ When the gate output falls

- Energy in capacitor is dumped to GND
- Dissipated as heat in the nMOS transistor
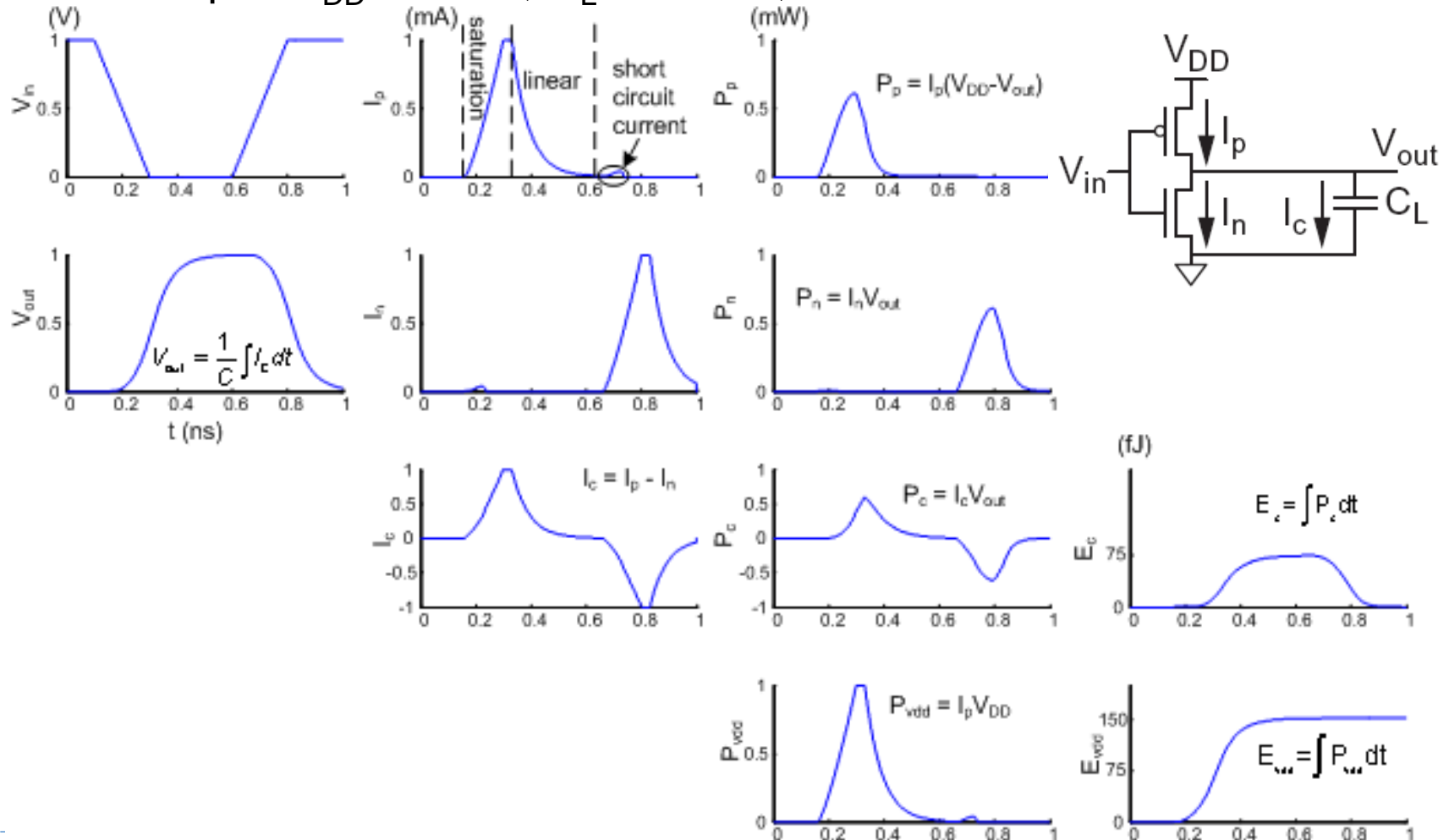
# Switching Waveforms


□ Example:  $V_{DD} = 1.0 \text{ V}$ ,  $C_L = 150 \text{ fF}$ ,  $f = 1 \text{ GHz}$



# Switching Power and Activity Factor

$$P_{\text{switching}} = \frac{1}{T} \int_0^T i_{DD}(t) V_{DD} dt = \frac{V_{DD}}{T} \int_0^T i_{DD}(t) dt = \frac{V_{DD}}{T} [T f_{\text{sw}} C V_{DD}]$$

$$= C V_{DD}^2 f_{\text{sw}}$$

 

Suppose the system clock frequency =  $f$ ,  $f_{\text{sw}} = \alpha f$  ( $\alpha$  = activity factor)

If the signal is a clock,  $\alpha = 1$

If the signal switches once per cycle,  $\alpha = 1/2$

$$\Rightarrow P_{\text{switching}} = \alpha C V_{DD}^2 f$$

$$P_{\text{dyn}} = C_L V_{DD}^2 \underbrace{f_{0 \rightarrow 1}}_{\text{Switching activity}}$$

the power consumption as the gate is switched on and off times per second

Switching activity 开关活动性

# Switching Power

---

Capacitance:  
function of fanout,  
wire length,  
transistor sizes

Supply voltage:  
scaling with  
generations

$$P_{\text{switching}} = \alpha C V_{DD}^2 f$$



Activity factor: how  
often on average  
wires switch

Clock frequency:  
scaling with  
generations


  
# Dissipation Due to Direct-Path Currents

- In actual designs, the assumption of the of the input wave forms is not correct. **zero rise and fall times**
- The finite slope of the input signal causes a **direct current** path between VDD and GND for a short period of time during switching, while the NMOS and PMOS are conducting simultaneously.
  - Leads to a blip of “short circuit” current.




$$E_{dp} = t_{sc} V_{DD} I_{peak}$$

$$P_{dp} = t_{sc} V_{DD} I_{peak} f = C_{sc} V_{DD}^2 f$$


$$t_{sc} = \frac{V_{DD} - 2V_T}{V_{DD}} t_s$$

# Short Circuit Currents

 

- Keep the input and output rise/fall times the same
- If  $V_{dd} < V_{tn} + |V_{tp}|$ , the short circuit power is eliminated since **both devices are never on at the same time**

 $I_{peak}$  depends on the saturation current of P/N MOS and the ration between input and output slopes ( $C_L$ )



# Dynamic Power Example

---


- 1 billion transistor chip
  - 50M logic transistors
    - Average width:  $12\lambda$
    - Activity factor = 0.1
  - 950M memory transistors
    - Average width:  $4\lambda$
    - Activity factor = 0.02
  - 1.0 V 65 nm process (with 50 nm drawn channel lengths and  $\lambda = 25$  nm)
  - $C = 1$  fF/mm (gate) + 0.8 fF/mm (diffusion)
- Estimate dynamic power consumption @ 1 GHz. Neglect wire capacitance and short-circuit current.

$$C_{\text{logic}} = (50 \times 10^6)(12\lambda)(0.025 \mu\text{m} / \lambda)(1.8 \text{ fF} / \mu\text{m}) = 27 \text{ nF}$$

$$C_{\text{mem}} = (950 \times 10^6)(4\lambda)(0.025 \mu\text{m} / \lambda)(1.8 \text{ fF} / \mu\text{m}) = 171 \text{ nF}$$

$$P_{\text{dynamic}} = [0.1C_{\text{logic}} + 0.02C_{\text{mem}}](1.0)^2(1.0 \text{ GHz}) = 6.1 \text{ W}$$

# Static Consumption

 

Sub-threshold current one of most compelling issues in low-energy circuit design!

Typical values in 65 nm


$I_{off} = 100 \text{ nA}/\mu\text{m} @ V_t = 0.3 \text{ V}$

$I_{off} = 10 \text{ nA}/\mu\text{m} @ V_t = 0.4 \text{ V}$

$I_{off} = 1 \text{ nA}/\mu\text{m} @ V_t = 0.5 \text{ V}$



$\eta = 0.1 \quad k_\gamma = 0.1$

$S = 100 \text{ mV/decade}$

 

Tunneling leakage from reverse-biased p-n junctions  
-- Between diffusion and substrate or well

# Static Consumption

  

Leakage control is critical for low-voltage operation


# Leakage Dependence on $V_t$

TSMC Processes Leakage and  $V_t$

	CL018 G	CL018 LP	CL018 ULP	CL018 HS	CL015 HS	CL013 HS
$V_{dd}$	1.8 V	1.8 V	1.8 V	2 V	1.5 V	1.2 V
$T_{ox}$ (effective)	42 Å	42 Å	42 Å	42 Å	29 Å	24 Å
$L_{gate}$	0.16 $\mu m$	0.16 $\mu m$	0.18 $\mu m$	0.13 $\mu m$	0.11 $\mu m$	0.08 $\mu m$
$I_{DSat}$ (n/p) ( $\mu A/\mu m$ )	600/260	500/180	320/130	780/360	860/370	920/400
$I_{off}$ (leakage) (pA/ $\mu m$ )	20	1.60	0.15	300	1,800	13,000
$V_{Tn}$	0.42 V	0.63 V	0.73 V	0.40 V	0.29 V	0.25 V
FET Perf. (GHz)	30	22	14	43	52	80

Exponential dependence

# Leakage Dependence on Temperature

 

# Putting it all together

---

$$P_{total} = P_{dyn} + P_{dp} + P_{stat}$$

become more and more important

$$= (C_L V_{DD}^2 + V_{DD} I_{peak} t_s) f_{0 \rightarrow 1} + V_{DD} I_{leak}$$

the dominant factor

can be kept within bounds  
by careful design





# Summary

---

- ☐ **Inverter Basic Characteristics**
- ☐ **Static Behavior**
  - **Voltage transfer Characteristics**
  - **Switching threshold**
- ☐ **Dynamic Behavior**
  - **Propagation Delay: First-order Analysis**
  - **Propagation Delay from Perspective**
- ☐ **Power, Energy**




# 集成电路原理与设计

## 11. 反相器

宋爽

shuangsonghz@zju.edu.cn

# Cascaded driver circuit

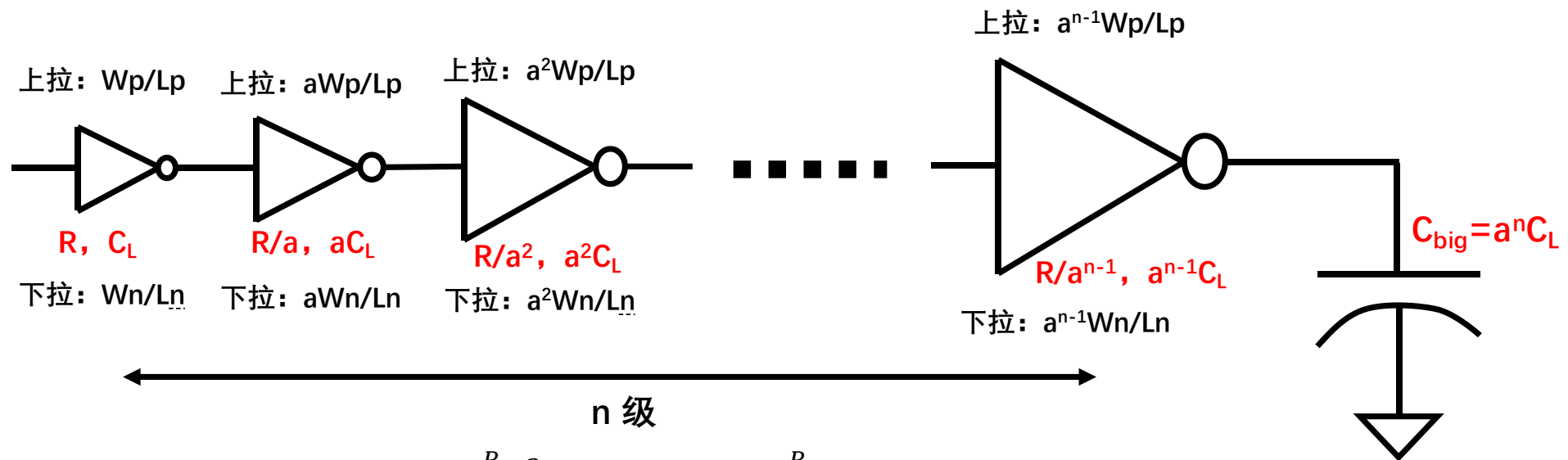

$$t_{tot} = -[\ln 0.5(RaC_L) + \ln 0.5(\frac{R}{a}a^2C_L) + \dots + \ln 0.5(\frac{R}{a^{n-1}}a^nC_L)]$$

$$= -n \ln 0.5(RC_L)$$

$$= nat_{min}$$

$$= n(\frac{C_{big}}{C_L})^{\frac{1}{n}} t_{min}$$

求最小值

$$\frac{dt_{tot}}{dn} = 0$$

最佳级数

$$n_{opt} = \ln(\frac{C_{big}}{C_L}) = \ln a^n$$

最优值  
 $a = e$


# Optimal sizing

---

- Use a chain of inverters, each stage has transistors a larger than previous stage.
- Minimize total delay through driver chain:
  - $t_{\text{tot}} = n(C_{\text{big}}/C_g)^{1/n} t_{\text{min}}$ .
- Optimal number of stages:
  - $n_{\text{opt}} = \ln(C_{\text{big}}/C_g)$ .
- Driver sizes are exponentially tapered with size ratio  $a$ .

# Layout example of buffers insertion

---

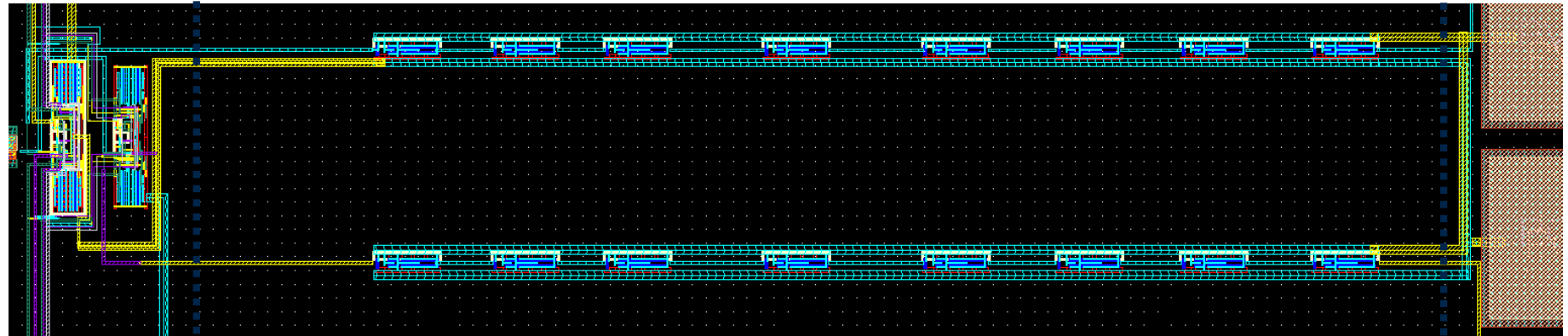

**Core terminals**

**Pads**

**Inserted buffers**

---