



## 习 题 5

Table 5.1

Parameter	Parameter Description	Typical Parameter Value		Units
		n-Channel	p-Channel	
$V_{T0}$	Threshold voltage( $V_{BS}=0$ )	0.7	-0.8	V
$K$	Transconductance parameter(in saturation)	134	50	$\mu A/V^2$
$\gamma$	Bulk threshold parameter	0.45	0.4	$V^{1/2}$
$\lambda$	Channel length modulation parameter	0.1	0.2	$V^{-1}$
$2 \phi_F $	Surface potential at strong inversion	0.9	0.8	V

5.1 Figure 5.1 shows an n-channel input differential amplifier, with the parameters shown in table 5.1. Consider  $I_{SS}=100\mu A$ (the drain current of M5), and  $W_1/L_1=W_2/L_2=W_3/L_3=W_4/L_4=W_5/L_5=1$ . Assuming all the channel lengths are equal to  $1\mu m$ , and  $V_{DD}=5V$ .

- (a) Calculate the differential transconductance  $g_{md}$  and the differential voltage gain  $A_v$   
 (b) Calculate the maximum ( $V_{IC(max)}$ ) and the minimum input common-mode voltages ( $V_{IC(min)}$ ), and the input common mode voltage range (ICMR)

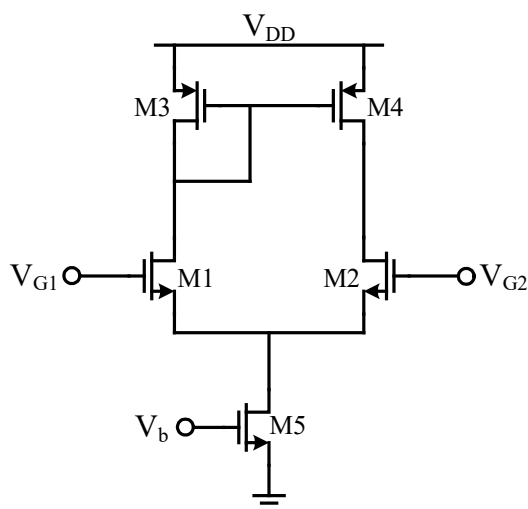


Figure 5.1

解:

(a)

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_4 = 1$$

$$g_{md} = g_{m1} = g_{m2} = \sqrt{K_n' \left(\frac{W}{L}\right)_1 I_{SS}} = 115.76\mu S$$

$$A_v = \frac{g_{m2}}{g_{ds2} + g_{ds4}} = \frac{2g_{m2}}{(\lambda_2 + \lambda_4)I_{SS}} = 7.72V/V$$

(b)

$$V_{IC(max)} = V_{DD} + V_{T1} - V_{T3} - V_{dsat3}$$

$$= V_{DD} + V_{T1} - V_{T3} - \sqrt{\frac{I_{SS}}{K'_p(W/L)_3}} = 3.49V$$

$$V_{IC}(\min) = V_{SS} + V_{T1} + V_{dsat1} + V_{dsat5}$$

$$= V_{SS} + V_{T1} + \sqrt{\frac{I_{SS}}{K'_N(W/L)_1}} + \sqrt{\frac{2I_{SS}}{K'_N(W/L)_5}} = 2.79V$$

$$ICMR = V_{IC}(\max) - V_{IC}(\min) = 0.7V$$

5.2 Find the value of the unloaded differential-transconductance,  $g_{md}$ , and the unloaded differential-voltage gain,  $A_v$ , for the p-channel input differential amplifier of Figure 5.3 when  $I_{SS}=10\mu A$  and  $I_{SS}=1\mu A$ . What is the slew rate of the differential amplifier if a 100 pF capacitor is attached to the output? Assuming  $W1/L1=W2/L2=W3/L3=W4/L4=1$ , and all the channel lengths are equal to  $1\mu m$ .

Use the transistor parameters of Table 5.1.

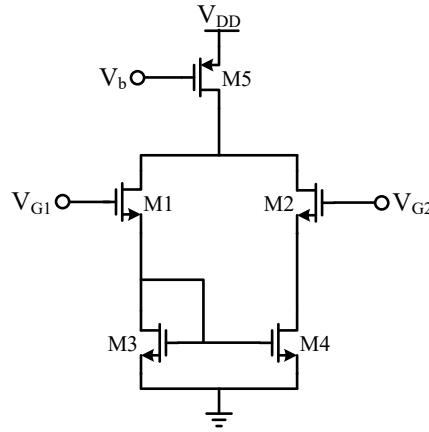


Figure 5.3

解:

a) Given  $I_{SS}=10\mu A$ ,

$$g_{md} = g_{m1} = g_{m2} = 36.6\mu S$$

$$A_v = \frac{g_{m1}}{g_{ds2} + g_{ds4}} = \frac{2g_{m1}}{(\lambda_1 + \lambda_2)I_{SS}} = 36.6V/V$$

Given  $I_{SS}=1\mu A$

$$g_{md} = g_{m1} = g_{m2} = 11.6\mu S$$

$$A_v = \frac{g_{m1}}{g_{ds2} + g_{ds4}} = \frac{2g_{m1}}{(\lambda_1 + \lambda_2)I_{SS}} = 115.8V/V$$

b) Slew rate can be given as

$$SR = \frac{I_{SS}}{C_L}$$

For  $I_{SS} = 10 \mu A$  and  $C_L = 100 \text{ pF}$

$$SR = \frac{I_{SS}}{C_L} = \underline{0.1 \text{ V}/\mu\text{s}}$$

For  $I_{SS} = 1 \mu A$  and  $C_L = 100 \text{ pF}$

$$SR = \frac{I_{SS}}{C_L} = \underline{0.01 \text{ V}/\mu\text{s}}$$

5.3 In the circuit of Fig 5.4, assume that  $I_{SS}=1\text{mA}$ ,  $V_{DD}=3\text{V}$  and  $W/L=50/0.5$  for all the transistors. And  $I_{D5}=I_{D6}=0.8(I_{SS}/2)$ . Assuming  $\lambda \neq 0$ .

(a) Determine the voltage gain.

(b) Calculate  $V_b$ .

(c) If  $I_{SS}$  requires a minimum voltage of  $0.4\text{V}$ , what is the maximum differential output swing?

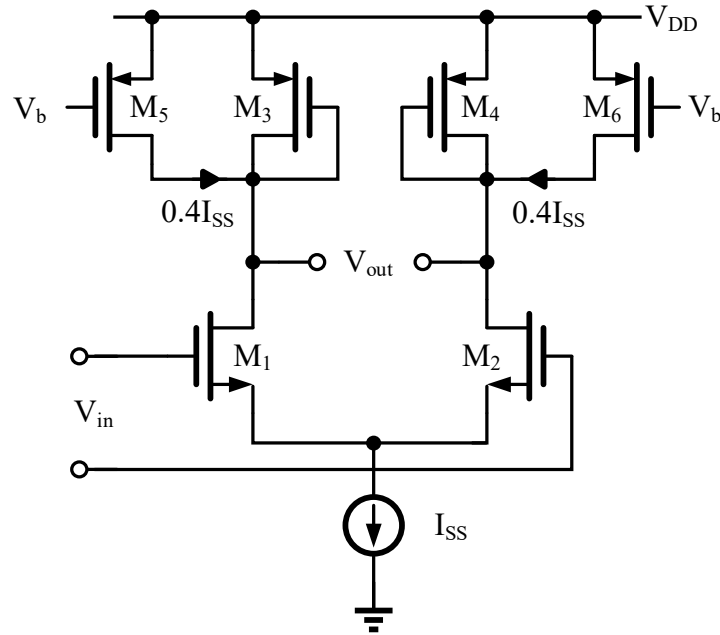


Figure 5.4

解:

$$a) A_v \approx -\frac{g_{m1}}{g_{m3}} = \sqrt{\frac{\mu_n I_{D1}}{\mu_p I_{D3}}} = \sqrt{\frac{134 \times 0.5 I_{SS}}{50 \times 0.2 \frac{I_{SS}}{2}}} = -3.66$$

$$b) I_{D5} = I_{D6} = 0.8 \frac{I_{SS}}{2} = 0.4 \text{ mA}$$

$$V_b = V_{DD} - V_{SG5} = V_{DD} - |V_{TH}| - \sqrt{\frac{2I_{D5}}{\mu_p C_{ox} \frac{W}{L}}} = 1.8V$$

c)

$$(V_{out1,2})_{\max} = \min(V_b + |V_{TH,P}|, V_{DD} - |V_{TH,P}|) = \min(1.9 + 0.8, 3 - 0.8) = 2.2V$$


$$(V_{out1,2})_{\min} = \max(V_{SS\min} + V_{GS1} \big|_{I_D=0.6I_{SS}} - V_{TH,N}, V_{DD} - V_{SG3} \big|_{I_D=0.2I_{SS}})$$

$$V_{GS1} \big|_{I_D=0.6I_{SS}} = V_{TH,N} + \sqrt{\frac{2 \times 0.6I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} = 0.7 + 0.3 = 1.0V$$

$$V_{SG3} \big|_{I_D=0.2I_{SS}} = |V_{TH,P}| + \sqrt{\frac{2 \times 0.2I_{SS}}{\mu_p C_{ox} \frac{W}{L}}} = 0.8 + 0.28 = 1.08V$$

$$(V_{out1,2})_{\min} = \max(0.4 + 1 - 0.7, 3 - 1.08) = 1.92V$$
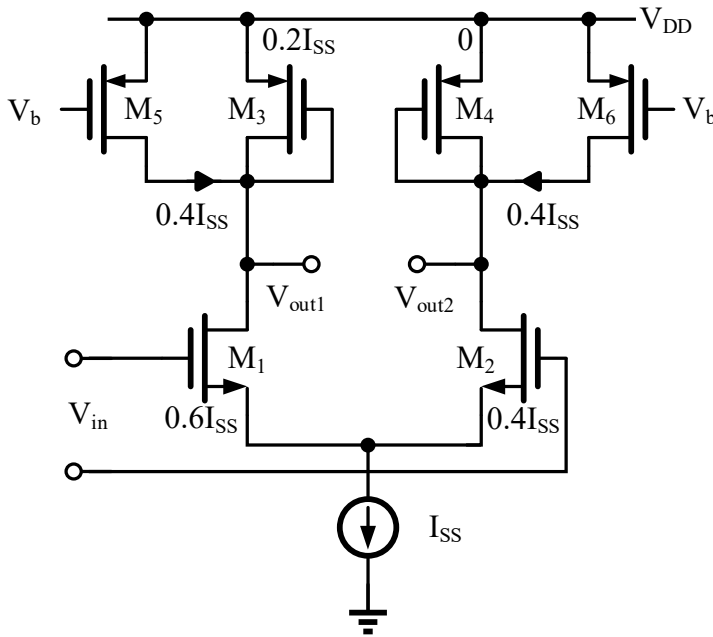
$$V_{out,swing} = 2(2.2 - 1.92) = 0.56V$$



5.4 The circuit shown in Figure 5.5 called a folded-current mirror differential amplifier and is useful for low values of power supply. Assume that all W/L values of each transistor is 100. **Using the parameters shown in table 5.1,**

- Find the maximum input common mode voltage,  $V_{IC}(\max)$  and the minimum input common mode voltage,  $V_{IC}(\min)$ . Keep all transistors in saturation for this problem.
- What is the input common mode voltage range, ICMR?
- Find the small signal voltage gain,  $v_{out}/v_{in}$ , if  $v_{in} = v_{I1} - v_{I2}$ .

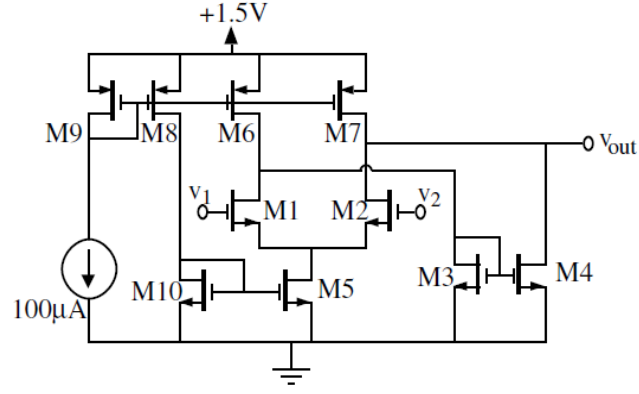


Figure 5.5

解：

$$\text{a) } v_{1(\max)} = V_{GS3} + V_{TN} = 0.7 + \sqrt{\frac{2 \cdot 50}{134 \cdot 100}} + 0.7 = 1.486V$$

$$\begin{aligned} v_{1(\min)} &= 0 + V_{DS5}(\text{sat}) + V_{GS1}(50\mu\text{A}) = \sqrt{\frac{2 \cdot 100}{134 \cdot 100}} + \left( \sqrt{\frac{2 \cdot 50}{134 \cdot 100}} + 0.7 \right) \\ &= 0.122 + 0.086 + 0.7 = 0.908V \Rightarrow v_{1(\min)} = 0.908V \end{aligned}$$

$$\text{b) } V_{ICMR} = v_{1(\max)} - v_{1(\min)} = 1.486 - 0.908 = 0.5784V$$

$$\text{c) } A_v = g_{m1} \times (r_{o2} // r_{o4} // r_{o7}) = 38.67V/V$$

5.5 In the circuit of Fig 5.5, assume that  $I_{SS} = 0.5\text{mA}$ ,  $V_{DD} = 3\text{V}$ ,  $(W/L)_{1,2} = 50/0.5$  and  $(W/L)_{3,4} = 10/0.5$ .  $I_{SS}$  current is provided by NMOS, and its  $W/L = 50/0.5$ . Assuming  $\lambda \neq 0$ .

- Calculate the range of input common mode voltage.
- If  $V_{in,CM} = 1.5\text{V}$ , draw a sketch of the small signal differential voltage gain of the circuit when  $V_{DD}$  changes from 0 to 3V.
- If the mismatch threshold voltage of  $M_1$  and  $M_2$  is  $1\text{mV}$ , calculate CMRR.
- If the  $W_3 = 10\mu\text{m}$  and  $W_4 = 11\mu\text{m}$ , calculate CMRR.

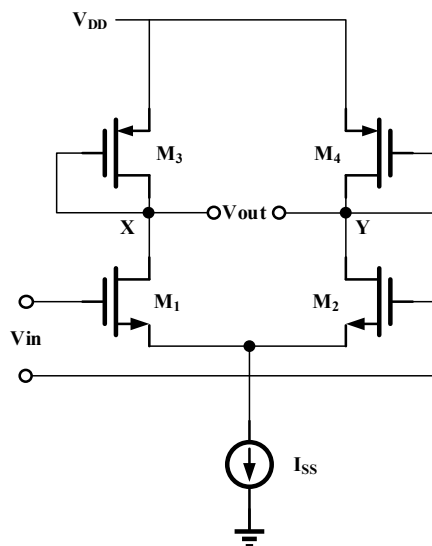


Figure 5.5

解:


$$a) \quad (V_{in,cm})_{\min} = V_{GS1} + V_{odss} = V_{TH1} + \sqrt{\frac{2I_{D1}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}} + \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_{SS}}} = 0.7\text{V} + 0.19\text{V} + 0.27\text{V} = 1.16\text{V}$$

$$(V_{in,cm})_{\max} = V_{DD} - V_{od3} - V_{TH,P} + V_{TH,N} = V_{DD} - 0.8 + 0.7 - \sqrt{\frac{2I_{D3}}{\mu_p C_{ox} \left(\frac{W}{L}\right)_3}} = 3\text{V} - 0.707\text{V} - 0.1 = 2.193\text{V}$$

- 三个标记点:

开启电压  $V_{TH,P} = 0.8\text{V}$
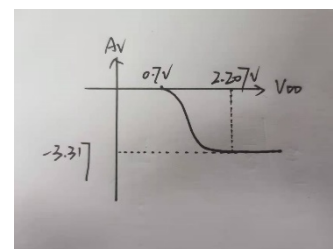
$$\text{增益 } A_v = -\sqrt{\frac{K_n \left(\frac{W}{L}\right)_1}{K_p \left(\frac{W}{L}\right)_3}} = -3.66$$



饱和点电压  $V_{DD} = V_{in,cm} - V_{TH,N} + V_{GS3} = 1.5\text{V} - 0.7\text{V} + 0.8\text{V} + 0.707\text{V} = 2.307\text{V}$  [图中数据有误]

c) 由于M1和M2的阈值电压失配，因此有：  $g_{m1} \neq g_{m2}, g_{m3} \neq g_{m4}$

为了计算 $A_{cm-dm}$ 有：

$$i_{D1} = g_{m1}(V_{in,cm} - V_p)$$

$$i_{D2} = g_{m2}(V_{in,cm} - V_p)$$


$$V_{out1} = -\frac{i_{D1}}{g_{m3}} = -\frac{g_{m1}(V_{in,cm} - V_p)}{g_{m3}}$$

$$V_{out2} = -\frac{i_{D2}}{g_{m4}} = -\frac{g_{m2}(V_{in,cm} - V_p)}{g_{m4}}$$

$$\frac{g_{m1}}{g_{m3}} = \sqrt{\frac{K_n(\frac{W}{L})_{1,2}}{K_p(\frac{W}{L})_{3,4}}} = \frac{g_{m2}}{g_{m4}}$$

$$\therefore V_{out1} = V_{out2}$$
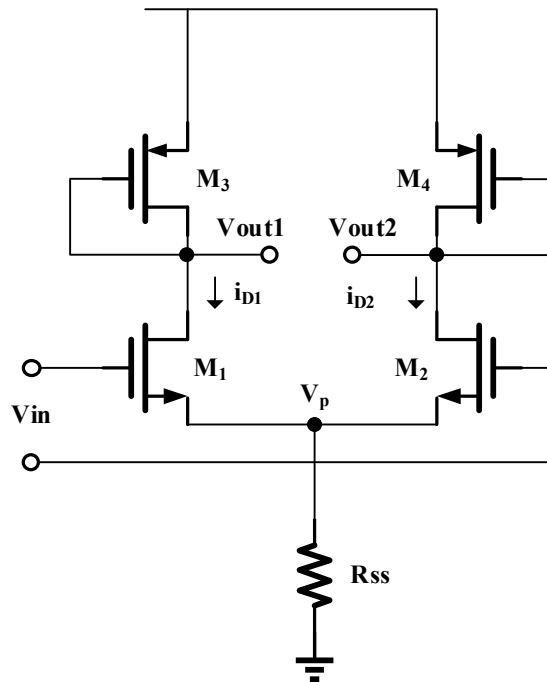
$$\therefore A_{cm-dm} = 0, CMRR = \infty$$



d)

$$A_{dm-dm} = -g_m R_D$$

$$A_{cm-dm} = \frac{g_m R_D}{1 + 2g_m R_{ss}} - \frac{g_m (R_D + \Delta R_D)}{1 + 2g_m R_{ss}} = -\frac{g_m \Delta R_D}{1 + 2g_m R_{ss}}$$

$$\therefore CMRR = \left| \frac{A_{dm-dm}}{A_{cm-dm}} \right| = \frac{1 + 2g_m R_{ss}}{\Delta R_D / R_D}$$

$$\therefore R_{D1} = \frac{1}{g_{m3}}, R_{D2} = \frac{1}{g_{m4}}$$

$$\therefore \frac{\Delta R_D}{R_D} = \frac{R_{D1} - R_{D2}}{R_{D1}} = 1 - \frac{R_{D2}}{R_{D1}} = 1 - \sqrt{\frac{2K_p(\frac{W}{L})_3 I_D}{2K_p(\frac{W}{L})_4 I_D}} = 1 - \sqrt{\frac{10}{11}} = 0.0465$$

$$gm = \sqrt{2Kn\left(\frac{W}{L}\right)_{I_{D1}}} = 2.59m\Omega^{-1}$$

$$R_{ss} = \frac{1}{\lambda I_{ss}} = \frac{1}{0.1 \times 0.5 \times 10^{-3}} = 20k\Omega$$

$$\therefore CMRR = \frac{1 + 2 \times 2.59m\Omega^{-1} \times 20k\Omega}{0.0465} = 2248$$