



Table 4.1

Parameter Symbol	Parameter Description	Typical Parameter Value		Units
		n-Channel	p-Channel	
$V_{T0}$	Threshold voltage ( $V_{BS} = 0$ )	$0.7 \pm 0.15$	$-0.7 \pm 0.15$	V
$K'$	Transconductance parameter (in saturation)	$110.0 \pm 10\%$	$50.0 \pm 10\%$	$\mu\text{A}/\text{V}^2$
$\gamma$	Bulk threshold parameter	0.4	0.57	$\text{V}^{1/2}$
$\lambda$	Channel length modulation parameter	$0.04 (L = 1 \mu\text{m})$ $0.01 (L = 2 \mu\text{m})$	$0.05 (L = 1 \mu\text{m})$ $0.01 (L = 2 \mu\text{m})$	$\text{V}^{-1}$
$2 \phi_F $	Surface potential at strong inversion	0.7	0.8	V

4.1 Calculate the output resistance and the minimum output voltage, while maintaining all devices in saturation, for the circuits shown in Figure 4.1. Assume that  $i_{\text{OUT}}$  is actually  $10\mu\text{A}$ . Use Table 4.1 for device model information.

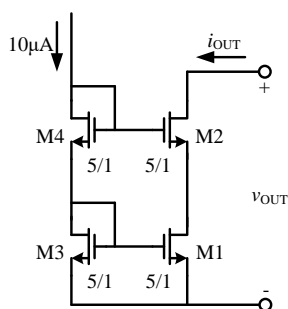


Fig 4.1

解:

$$V_{GS3} = V_{G3} = \sqrt{\frac{2i_D}{\beta}} + V_T = \sqrt{\frac{2 \times 10 \times 10^{-6}}{5 \times 110 \times 10^{-6}}} + 0.7 = \sqrt{\frac{20}{550}} + 0.7 = 0.891$$

$$V_{SB2} = V_{G3} = 0.891$$

$$V_{DS1} = V_{G3} + V_{GS4} - V_{GS2} \text{ because all devices are matched.}$$

$$g_{m2} = g_{m4} \cong \sqrt{(2KW/L)|I_D|} = \sqrt{2 \times 110 \times 10^{-6} \times 5/1 \times 10 \times 10^{-6}} = 104.9 \times 10^{-6}$$

$$g_{mbs2} = g_{mbs4} = g_{m2} \frac{\gamma}{2(2|\phi_F| + V_{SB})^{1/2}} = 104.9 \times 10^{-6} \frac{0.4}{2(0.7 + 0.891)^{1/2}} = 16.63 \times 10^{-6}$$

$$r_{out} = \frac{v_{out}}{i_{out}} = r_{ds1} + r_{ds2} + [(g_{m2} + g_{mbs2})r_{ds2}] r_{ds1}$$

$$g_{ds1} = g_{ds2} \cong I_D \lambda = 10 \times 10^{-6} \times 0.04 = 400 \times 10^{-9}$$

$$r_{ds1} = r_{ds2} = \frac{1}{g_{ds}} = 2.5 \times 10^6$$

$$r_{out} = 2.5 \times 10^6 + 2.5 \times 10^6 + [(104.9 \times 10^{-6} + 16.63 \times 10^{-6}) 2.5 \times 10^6] 2.5 \times 10^6$$

$$r_{out} = 764 \times 10^6$$

$$\begin{aligned} v_{out(min)} &= V_{GS3} + V_{GS4} - V_{T2} = V_{GS3} + \sqrt{\frac{2i_D}{\beta}} + V_{T4} - V_{T2} \\ &= V_{GS3} + \sqrt{\frac{2i_D}{\beta}} = 0.891 + \sqrt{\frac{2 \times 10 \times 10^{-6}}{5 \times 110 \times 10^{-6}}} = 1.082 \text{V} \end{aligned}$$

4.2 Design M3 and M4 of Figure 4.2(a) so that the output characteristics are identical to the circuit shown in Figure 4.2(b). It is desired that  $i_{OUT}$  is ideally 10uA.

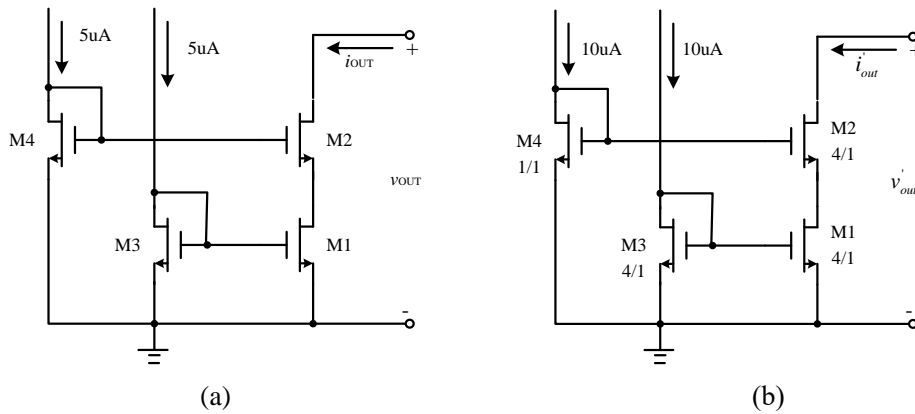


Figure 4.2

解:

For getting  $i'_{out} = i_{out} = 10\mu A$

In Fig.4.2a),  $\therefore i_3 = i_4 = 5\mu A$

Thus to ensure  $i_{out} = 10\mu A$

We must have  $\left(\frac{W}{L}\right)_1 = 2\left(\frac{W}{L}\right)_3$

$$\left(\frac{W}{L}\right)_3 = \frac{1}{2}\left(\frac{W}{L}\right)_1 = \frac{1}{2} \cdot \frac{4}{1} = \frac{2}{1}$$

In Fig. 4.2b)  $i_4 = i_3 = i_1$

$$\left(\frac{W}{L}\right)_4 \Delta V_4^2 = \left(\frac{W}{L}\right)_1 \Delta V_1^2 \Rightarrow \left(\frac{1}{1}\right) \Delta V_4^2 = \left(\frac{4}{1}\right) \Delta V_1^2$$

$$\therefore \frac{\Delta V_4^2}{\Delta V_1^2} = \frac{4}{1} \Rightarrow \Delta V_4 = 2\Delta V_1$$

$$V_{G4} = V_T + 2\Delta V_1$$

$$V_{G2} = V_{G4} = V_T + 2\Delta V_1$$

$$\therefore V_{MIN} = 2\Delta V_1$$

And we get  $V_{MIN}$  in Fig.5.2(a):  $V_{MIN} = 2\Delta V_1$

$$\therefore V_{G2} = V_{G4} = V_T + 2\Delta V_1 \quad \text{and} \quad \Delta V_4 = 2\Delta V_1$$

In Fig.5.2(a):  $i_4 = i_3 = \frac{1}{2}i_1$

$$\left(\frac{W}{L}\right)_4 \Delta V_4^2 = \frac{1}{2}\left(\frac{W}{L}\right)_1 \Delta V_1^2$$

$$\left(\frac{W}{L}\right)_4 = \frac{1}{2}\left(\frac{W}{L}\right)_1 \left(\frac{\Delta V_1}{\Delta V_4}\right)^2$$

$$\text{For } \left(\frac{\Delta V_4}{\Delta V_1}\right)^2 = 4 \Rightarrow \left(\frac{\Delta V_1}{\Delta V_4}\right)^2 = \frac{1}{4}$$

$$\left(\frac{W}{L}\right)_4 = \frac{1}{8}\left(\frac{W}{L}\right)_1 = \frac{1}{8} \cdot \frac{4}{1} = \frac{1}{2}$$

4.3 A reference circuit is shown in figure 4.3, assume that  $(W/L)_1 = (W/L)_2 = (W/L)_3 = 4$ ,  $(W/L)_4 = 1$ , please calculate the expression of  $V_{REF}$ .

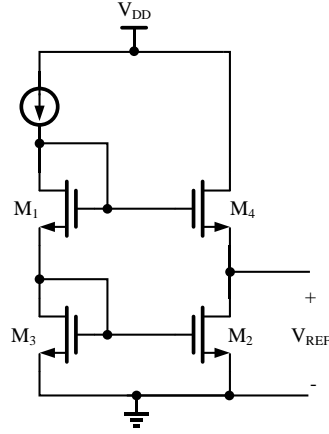


Figure 4.3

解:

$V_T$

4.4 As the circuits shown in Figure 4.4,  $I_{REF}=0.3\text{mA}$  and  $\gamma=0$ . Using the model parameters in Table 4.1,

(a) Calculate the voltage  $V_b$  when  $V_X=V_Y$ ;

(b) If  $V_b$  is 100mV smaller than the value in (a), calculate the deviation of  $I_{out}$  from  $300\text{ }\mu\text{A}$ .

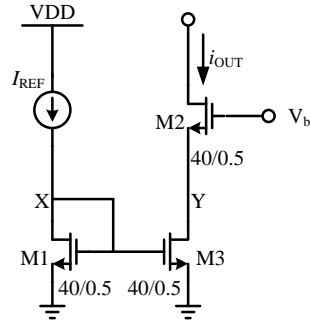


Figure 4.4

解:

a)

$$V_{GS1} = V_T + \sqrt{\frac{2I_{REF}}{K_N'(W/L)_1}} = 0.7 + \sqrt{\frac{2 \times 0.3 \times 10^{-3}}{80 \times 110 \times 10^{-6}}} = 0.961\text{V}$$

$$V_b = 2V_{GS1} = 1.922\text{V}$$

b)

$$\lambda(l = 0.5\text{ }\mu) \approx \lambda(l = 1\text{ }\mu) \frac{1\text{ }\mu}{0.5\text{ }\mu} = 0.04 \times 2 = 0.08\text{V}^{-1}$$

$$I_{out} = I_{REF} \frac{1 + \lambda(V_{GS1} + \Delta V_b)}{1 + \lambda V_{GS1}}$$

$$\Delta I_{out} = I_{REF} \frac{\lambda \Delta V_b}{1 + \lambda V_{GS1}} = 0.3 \times 10^{-3} \times \frac{0.08 \times (-0.1)}{1 + 0.08 \times 0.961} = -2.229 \times 10^{-6}\text{ A}$$

4.5 Assume that  $W/L$  ratios of Figure 4.5 are  $(W/L)_1 = 2\mu\text{m}/1\mu\text{m}$  and  $(W/L)_2 = (W/L)_3 = (W/L)_4 = 1\mu\text{m}/1\mu\text{m}$ . Find the dc value of  $v_{IN}$  that will give a dc current in M1 of  $110\mu\text{A}$ . Calculate the small signal voltage gain and output resistance using the parameters of Table 4.1. Assume  $\lambda=\gamma=0$ .

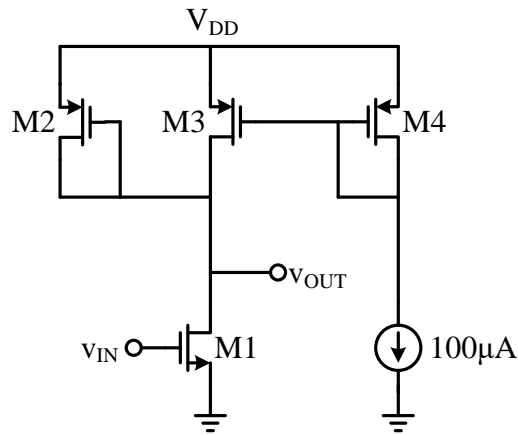


Figure 4.5

Solution:

$$I_{D1} = \frac{1}{2} K'_N \left( \frac{W}{L} \right)_1 (V_{in} - V_{TH1})^2$$

$$110\mu = \frac{1}{2} \times (110\mu) \times \frac{2}{1} \times (V_{in} - 0.7)^2$$

$$V_{in} = 1.7V$$

$$I_{D3} = I_{D4} = 100\mu A$$

$$I_{D2} = I_{D1} - I_{D3} = 10\mu A$$

$$A_v \cong -\frac{g_{m1}}{g_{m2}} = -\frac{\sqrt{K'_N (W/L)_1 I_{D1}}}{\sqrt{K'_P (W/L)_2 I_{D2}}} = -\frac{\sqrt{110\mu \times \frac{2}{1} \times \frac{110\mu}{10\mu}}}{\sqrt{50\mu \times 1 \times 10\mu}} = -6.96V/V$$

$$R_{out} \cong \frac{1}{g_{m2}} = \frac{1}{\sqrt{2K'_P (W/L)_2 I_{D2}}} = \frac{1}{\sqrt{2 \times 50 \times 10^{-6} \times 1 \times 10 \times 10^{-6}}} = 31.6K\Omega$$